VCD-8/11/14 - FYIT - DC- SEM 1 75 MARKS - 2 1/2 HRS

Note: 1.All questions are compulsory.

- 2. Figure should be neat and labeled.
- 3. Write side indicates full marks.

Q.1 Attempt any 2 from the following.

(10 M)

1. Solve the following.

- 1. $(4567)_8 = (?)_2$
- 11. $(1011011011111)_2 = (?)_8$
- 2. Solve the following.
 - $(111001)_2 * (111)_2 = (?)_2$
 - $(111010)_2 / (1001)_2 = (?)_2$ 11.
- 3. Represent the following number in signed magnitude, BCD, Excess-3, Gray code.
 - 1. $(125)_{10}$
 - II. $(234)_{10}$
- 4. Solve the following using 2's compliment method.
 - $(4-10)_{10}$

Q.2 Attempt any 2 from the following.

(10 M)

- 1. Construct basic gates using NOR gates.
- 2. Explain De'Morgons 2'nd law.
- 3. Write short note on Gates.
- 4. Realize the equation, draw the K-Map & circuit diagram by using SOP method. $F(A,B,C,D)=\sum M(0,1,2,3,8,9,10,11,12,13)$ Silip

Q.3 Attempt any 2 from the following.

(10 M)

- 1. Write short note on half Adder.
- 2. Explain encoder.
- 3. Write short note on full Subtractor.
- 4. Draw 16:1 multiplexer for the following.

$$Y = \sum_{m} m(1, 2, 5, 7, 9, 11, 13)$$

Q.4 Attempt any 2 from the following.

(10 M)

- 1. Write short note on D-type and T-type Flip-Flop.
- 2. Explain S-R Flip-Flop.
- 3. Write short note on Shift Registers.
- 4. Write short note on Counters.

Q.5 Attempt any 2 from the following.

(10 M)

- 1. Write short note on Basic Organization of Computers.
- 2. Write short note on Memory.
- 3. Write short note on Secondary Memory. (Hard Disk & Optical disk)
- 4. Write short note on Cache Memory.