

NOTE: ALL QUESTIONS ARE COMPULSORY.

DRAW A NEAT AND LABELED DIAGRAM WHEREVER NECESSARY.

Q1] Solve the Following.

- A. Draw and explain symbol and truth table for EX-OR gate. [5]
- B. Explain S-R Flip-Flop. [5]

Q2] Attempt any 3 from the following.

- A. Solve the following. [5]  
 $(ABC.12)_{16} = (?)_2$
- B. Perform  $(12-6)_{10}$  using 2's compliment method. [5]
- C.  $(0101111)_2 + (0111001)_2 + (1010111)_2 = (?)_2$  [5]
- D.  $(1011)_2 * (1110)_2 = (?)_2$  [5]

Q3] Attempt any 3 from the following.

- A. Construct Basic Gates using NAND gates. [5]
- B. Explain De'Morgans 1<sup>st</sup> law. [5]
- C. Realize the equation, Draw the K-Map & circuit diagram by using SOP method. [5]  
 $F(A,B,C,D) = \sum m(0,1,2,3,8,9,10,11,12,13)$
- D. Write short note on basic Gates. [5]

Q4] Attempt any 3 from the following.

- A. Write short note on Half Adder. [5]
- B. Explain Binary To Gray Code Converter. [5]
- C. Write short note on Encoder. [5]
- D. Draw 8:1 Multiplexer for the following. [5]  
 $y = \sum m(1, 2, 4, 5, 6, 7)$

Q5] Attempt any 3 from the following.

- A. Write short note on Shift Registers. [5]
- B. Write short note on J-K Flip-Flop. [5]
- C. Write short note on D-type and T-type Flip-Flop. [5]
- D. Write short note on Counters. [5]

Q6] Attempt any 3 from the following.

- A. Write short note on I/O Devices. [5]
- B. Write short note on Hard Disk. [5]
- C. Write short note on Optical Disk. [5]
- D. Write short note on Secondary Memory. [5]

Q7] Attempt any 3 from the following.

- A. Write short note on Single User/Single tasking Operating System. [5]
- B. Write short note on Multi User/Multitasking Operating System. [5]
- C. Write short note on Real Time Operating System. [5]
- D. Write short note on Linux Operating System. [5]