

- Note: i) All the questions are compulsory.
 ii) Figures to the right indicate full marks.
 iii) Use of non programmable calculator is allowed.

Q.1.A] Select the correct option:

[12M]

- 1) A differential amplifier _____.
 (a) Rejects common-mode signals (b) Amplify differential-mode signals
 (c) Both (a) & (b) (d) Accept two input signals & amplify them.
- 2) An amplifier has a power gain of 100. Its dB gain is _____.
 (a) 20dB (b) 40dB (c) 10dB (d) none
- 3) The volume of a sphere of radius $3R$ is _____.
 (a) $\frac{4}{3}\pi R^3$ (b) $2\pi R^3$ (c) $36\pi R^3$ (d) none
- 4) If the value of the collector current I_C increases in CE configuration, then value of V_{CE} _____.
 (a) remains same (b) decreases (c) increases (d) none
- 5) The value of the line integral $\int \text{grad}(x+y-z) dr$ from $(0,1,-1)$ to $(1,2,0)$ is _____.
 (a) -1 (b) 3 (c) 0 (d) none
- 6) The work done by the force $\vec{F} = yz\hat{i} + zx\hat{j} + xy\hat{k}$ in moving a particle from point $(1,1,1)$ to $(3,3,2)$ along a path is _____.
 (a) 51 (b) 0 (c) 17 (d) none

Q.1.B] Answer in one statement:

[3M]

1. What happens in case of cutoff region operation.
2. Give unit vector in the direction of $\vec{A} = 2\hat{i} + 2\hat{j} - \hat{k}$.
3. Which IC is used to study Op-Amp?

Q.1.C] Fill in the blanks:

[5M]

- 1) A necessary & sufficient condition that line integral $\oint \vec{A} \cdot d\vec{r} = 0$ for every close curve C is _____.
- 2) Volume element in cylindrical system is _____.
- 3) The stability factor value for the base resistor bias is _____.
- 4) In sustaining oscillations, the loop gain should be _____.
- 5) The phase difference between the output & input voltages of CE amplifier is _____.

Q.2.A] Attempt any one: -

[8M]

1. Evaluate using cylindrical co-ordinates: $\int_0^{2\pi} \int_0^3 \int_0^{z/3} r^3 dr dz d\theta$

2. S is the surface of the plane $2x+y+2z=3$ in the first octant. Evaluate $\int \vec{A} \cdot \vec{n} dS$ if $\vec{A} = (x^2+y^2)\hat{i} - 2x^2\hat{j} + 2yz\hat{k}$.

By using the divergence theorem evaluate $\iint \vec{F} \cdot \vec{n} dS$

where $\vec{F} = 3xz\hat{i} + 2y^2\hat{j} + yz\hat{k}$ & S is surface of the cube bounded by $x=0$ to 1 , $y=0$ to 1 & $z=0$ to 1

Q.2.B] Attempt any one: -

[8M]

1. Evaluate using spherical co-ordinates: $\int_0^{2\pi} \int_0^\pi \int_0^{(1-\cos\phi)/2} r^2 \sin\phi dr d\phi d\theta$
2. Check the fundamental theorem for gradients using $T=x^2+4xy+2yz^3$ the points $A=(0,0,0), B=(1,1,1)$ and the three paths,
 - i) $(0,0,0) \rightarrow (1,0,0) \rightarrow (1,1,0) \rightarrow (1,1,1)$
 - ii) $(0,0,0) \rightarrow (1,0,0) \rightarrow (1,1,0) \rightarrow (1,1,1)$
 - iii) The parabolic path $z=x^2, y=x$

Q.2.C] Attempt any one: -

[4M]

1. State fundamental theorem of Curls with diagram.
2. Show that $\frac{\partial r}{\partial r} \cdot \frac{\partial r}{\partial \theta} = \frac{\partial r}{\partial \phi} \cdot \frac{\partial r}{\partial \theta} = \frac{\partial r}{\partial \theta} \cdot \frac{\partial r}{\partial \phi} = 0$ when $x=r \sin\theta \cos\phi, y=r \sin\theta \sin\phi, z=r \cos\theta$ are the spherical co-ordinates.

Q.3.A] Attempt any one: -

[8M]

1. Explain any four advantages of Negative Feedback.
2. Describe dc bias circuit with Emitter resistor for a transistor. Determine its stability factor. State its advantages.

Q.3.B] Attempt any one: -

[8M]

1. Describe Voltage divider biasing for a transistor. Determine its stability factor. State its advantages & disadvantages.
2. What is faithful amplification? State and explain any two conditions to be fulfilled to achieve faithful amplification in a transistorized amplifier.

Q.3.C] Attempt any one: -

[4M]

1. A power amplifier has an input voltage $v_i=12V$ peak to peak & an output voltage $v_o=8V$ peak to peak across a load resistance of 8Ω . The amplifier input resistance is $500K\Omega$. Determine its power gain.
2. Define amplifier. An amplifier has an input signal voltage $0.1V$ & draws $0.1mA$ from the source. The amplifier delivers $5V$ to a load at $10mA$. Determine the voltage, current and power gain.

Q.4.A] Attempt any one: -

[8M]

1. Draw labeled diagram of Colpitts oscillator & using this diagram determine the following parameters:
 - a) feedback fraction
 - b) min. gain for sustain oscillations
 - c) freq. of oscillation.
- Use the foll. Components: $C_1=0.014\mu F, C_2=0.14\mu F, L=20\mu H$.

2. By means of a neat circuit diagram explain the use of Op-amp as a Inverting amplifier. What is the input resistance of Op-amp used as inverting amplifier when its output is -12V, with input of 120mV. The feedback resistance is $10M\Omega$.

[8M]

Q.4.B] Attempt any one: -

1. Explain the basic requirements of Sustained oscillations. Determine the operating frequency & feedback factor for Hartley oscillator, using the following data: $L_1=200mH, L_2=2000mF, M=0.002mH, C=20pF$

2. Explain the architecture block diagram of a typical Op-amp. Calculate the output voltage of an Op-amp working as a differentiator; A ramp of 3V height drives the circuit and has width of 3msec. If the R_fC time constant is 1 msec. for $C=0.1\mu F$

[4M]

Q.4.C] Attempt any one: -

1. Write a note on Hartley Oscillator.

2. Determine the output voltage of a non-inverting amplifier for $R_i=200K, R_f=2M\Omega$ & input voltage 10mV.

[20M]

Q.5] Answer the following: -[Any four]

1. Explain an oscillator with a simple block diagram.

2. By means of a neat circuit diagram explain the use of Op-amp as a Non-inverting amplifier.

3. Determine the volume integral of the function $T=z^2$ over the tetrahedron with corners at $(0,0,0), (1,0,0), (0,1,0)$ & $(0,0,1)$.

4. A solid of constant density $\rho=1$ occupies the region S. Find the solids M.I. about z-axis. Given: $r \leq 1$ by the cone $\phi=\pi/3$

5. It is desired to set the operating point at 4V, 1.2 mA by biasing silicon transistor with collector feedback resistor R_B . If $\beta = 120$, find the value of R_B .

6. Determine the open circuit voltage of the source, v_s to provide an amplifier input voltage v_i of 0.25V when the internal resistance of the source is 50Ω .

-X-X-X-X-X-X-X-X-X-X-X-X-X-X-