

- Note: 1) All questions are compulsory.
- 2) Figures to the right indicate full marks.
- 3) Use of non-programmable calculator is allowed.
- 4) Symbols have their usual meanings.

Q. 1 (A) Chose correct alternative among the four and rewrite the statement. (12)

- 1) The gradient of a function ($\sin x + \sin y$) is _____.
 - a) $\cos x \hat{i} - \sin y \hat{j}$
 - b) $\cos x \hat{i} + \sin y \hat{j}$
 - c) $\sin x \hat{i} - \cos y \hat{j}$
 - d) $\sin x \hat{i} + \cos y \hat{j}$
- 2) The scalar factor of spherical co-ordinates is _____.
 - a) 1, r, r sin θ
 - b) 1, r, r
 - c) r, r, 1
 - d) r, 1, r
- 3) If base emitter junction is forward biased and base collector junction is reversed biased then operation of transistor is in _____.
 - a) active region
 - (b) saturated region
 - (c) cut-off region
 - (d) none of these
- 4) An amplifier has a power gain of 100. Its dB gain is _____.
 - (a) 20 dB
 - (b) 40 dB
 - (c) 10 dB
 - (d) none of these
- 5) When we introduce positive feedback to an amplifier the Gain - bandwidth product ----
 - a) Increases
 - b) decreases
 - C) remains the same.
 - D) can increase or decrease
- 6) Which of the following is required for oscillation?
 - a) $\beta A_v > 1$
 - b) The phase shift around the feedback network must be 0° or 360° .
 - c) Both $\beta A_v > 1$ and the phase shift around the feedback network must be 0° or 360° .
 - d) None of the above

Q. P. Code:-20511**Q. 1 (B)** Answer the following questions in one statement.**(03)**

- 1) Express the unit vectors \hat{r} , $\hat{\theta}$, $\hat{\phi}$ in terms of cartesian coordinate system
- 2) What is meaning of phase reversal?
- 3) What is Op-Amp comparator?

Q. 1 (C) Fill in the blanks.**(05)**

- 1) The line integral is also known as _____ integral.
- 2) Co-ordinate ϕ is the azimuth angle of the plane containing the point P and _____ axis; measured from XZ plane in the right hand screw sense.
- 3) It should be ensured that collector emitter voltage not fall below _____ V for silicon transistor.
- 4) A voltage follower has a voltage gain of _____.
- 5) In an ideal op-amp integrator if the input is square wave then the output waveform will be _____.

Q. 2. (A) Attempt any One**(08)**

- 1) State and explain fundamental theorem for curl. Give its geometrical and physical interpretation. Give one example
- 2) Verify Stoke's theorem for the function $\vec{F} = x(x\hat{i} + y\hat{j})$, integration round the square in the plane $Z=0$ whose sides are along the lines $x=0$, $y=0$, $x=a$ and $y=a$

Q. 2 (B) Attempt any One**(08)**

- 1) With the help of diagram explain cylindrical polar co-ordinates.
- 2) Obtain an expression for the divergence of a vector function in spherical polar co-ordinates.

Q. 2 (C) Attempt any One**(04)**

- 1) Obtain expression for infinitesimal surface area of a sphere of radius 'r' and centre at origin.
- 2) Find total work-done by the force $\vec{F} = (zy\hat{i} + xy\hat{j})$ N in moving a particle along the straight line path from O (0,0) to P (2, 1).

3. (a) Attempt any One

(8)

- (i) Draw voltage divider bias circuit and its Thevenin equivalent circuit. Obtain the expressions for V_{TH} and R_{TH} , base current I_B , collector voltage V_C , V_{CE} , collector current I_C , stability factor S .
- (ii) Explain the effect of negative feedback on stability, distortion and output resistance of an amplifier.

3. (b) Attempt any One

(8)

- (i) A base bias circuit is subjected to an increase in temperature from 25°C to 75°C . If $\beta = 100$ at 25°C and $\beta = 150$ at 75°C , determine the percentage change in Q-point values (I_C and V_{CE}) over this temperature neglecting change in V_{BE} and leakage current. Given: $V_{CC} = 9\text{ V}$, $R_B = 200\text{ k}\Omega$ and $R_C = 1\text{ k}\Omega$
- (ii) Write general theory of feedback.

3. (c) Attempt any One

(4)

- (i) Explain the concept of thermal runaway.
- (ii) An amplifier has an input signal voltage $V_i = 0.2\text{ V}$ and draws 1 mA from the source. The amplifier delivers 10 V to a load at 25 mA . Determine voltage and current gain.

Q.4 A Attempt Any One

(8)

- i Draw circuit of RC phase shift oscillator using BJT. Derive the expression for the frequency of oscillation.
- ii Describe with neat circuit diagram working of Colpitt's oscillator. Derive the expression for the frequency of oscillation.

B Attempt Any One

(8)

- i Explain, with neat circuit diagram, the non-inverting amplifier using OPAMP and derive the expression for the Output Voltage.
- ii Describe with neat circuit diagram OPAMP integrator. What is critical frequency of an integrator?

C Attempt Any One

(4)

- i A Hartley oscillator produces an output at a frequency of 100 KHz . Given $L_1 = L_2 = L$ and $C = 0.001\text{ }\mu\text{F}$. find the value of L .
- ii Calculate the value of C and feedback resistor R_f for a typical Wien-bridge oscillator, if $R = 7950\text{ }\Omega$, $R_1 = 10\text{ K}\Omega$ and oscillator frequency of 2 KHz .

Q. 5 Attempt any Four

(20)

- 1) Write a note on Surface integrals
- 2) Obtain the expression for gradient of a scalar function in terms of cylindrical co-ordinates.
- 3) Write a short note on proper zero signal collector current
- 4) Explain the concept of input resistance of an amplifier.
- 5) An op-amp is used as 3 input inverting adder with $R_i = R_f = 5 \text{ K}\Omega$ $V_1 = +1.0\text{V}$ $V_2 = -2\text{V}$ and $V_3 = +4.5\text{V}$ find the output voltage. If the R_i value is reduced to $2 \text{ K}\Omega$, keeping R_f the same, what will be new output voltage?
- 6) Determine the maximum frequency that may be used in op-amp with slew rate of $1\text{V}/\mu\text{s}$. The amplifier circuit has $R_f = 200\text{K}\Omega$ and $R_i = 10 \text{ K}\Omega$ and input voltage $V_i = 0.02 \text{ V}$ having angular frequency of $3 \times 10^5 \text{ rad/s}$. State whether this input will give distorted output or not.

-----THE END.-----