

Note: i) All the questions are compulsory.

ii) Figures to the right indicate full marks.

iii) Use of non programmable calculator is allowed.

Q1 : Answer the following questions:

- A) Convert the following into SOP form  $F(a,b,c) = \sum m(0,5,6,7)$  and draw logical circuit diagram. (7M)

OR

- A) Convert the following into POS form  $F(a,b,c) = \prod M(0,1,5,6)$  and draw logical circuit. (7M)

- B) Convert the following (8M)

i)  $(B4D)_{16} = (?)_8$

ii)  $(10101.10)_2 = (?)_{10}$

OR

- B) Perform  $A+B$ ,  $A-B$  &  $-A-B$  using 2's complement method where  $A=43$ ,  $B=29$
- C) Draw & explain the working of RS flipflop. (5M)

OR

- C) Perform the following in binary arithmetic (5M)

i)  $11110.11 + 111.1101$

ii)  $11011 \times 101.1$

iii)  $11001 \times 101$

iv)  $1011101 + 0111010$

v)  $11001 \div 101$

Q2 : Answer the following questions:

- A) With the help of neat labelled diagram explain the operation of RC phase shift oscillator. A phase shift oscillator has  $R=5 \text{ K}\Omega$ ,  $C=0.001 \mu\text{F}$ . Find the frequency of oscillation. (7M)

OR

- A) With the help of neat labelled diagram explain the operation of colpitt's oscillator. A colpitt's oscillator is designed by using components  $C_1=0.02 \mu\text{f}$ ,  $C_2=0.002 \mu\text{F}$  &  $L=10 \mu\text{H}$ . Calculate oscillating frequency. (7M)

- B) With the help of neat labelled diagram obtained the expression for output voltage of summing amplifier? OP-amp as inverting adder determine feedback resistor  $R_f$  if  $V_1=0.9\text{V}$ ,  $V_2=1.2\text{V}$ ,  $V_3=2.0\text{V}$  for  $R_1=3\text{M}\Omega$ ,  $R_2=4\text{M}\Omega$  and  $R_3=6\text{M}\Omega$ . (8M)

OR

- B) Derive the expression for gain of Op-amp as a inverting amplifier. What is input resistance of OP Amp used as inverting amplifier when its output is  $-12\text{V}$ . With input of  $120\text{mV}$ . The feedback resistor is  $10\text{M}\Omega$ . (8M)

- C) Explain the block diagram of OP-Amp amplifier (5M)

OR

- C) What is oscillator? Explain the requirement for oscillator. (5M)



Q3 : Answer the following questions:

A) Describe with neat diagram stability factor of collector to base resistor method for transistor biasing. (7M)

OR

A) Explain frequency response of an amplifier. What are lower cut off frequency ( $f_l$ ) and higher cut off frequency ( $f_h$ ) of an amplifier? What is relation of bandwidth in terms of  $f_l$  &  $f_h$ ? (7M)

B) What is faithful amplification? State & explain the condition to be fulfilled to achieve faithful amplification in a transistorized amplifier. (8M)

OR

B) Draw and explain black box representation of amplifier circuit & write all amplifier notations. (8M)

C) What is feedback amplifier? State various types of feedback? (5M)

OR

C) What is stabilization? What is need for stabilization? (5M)

Q4 : Answer the following questions (any 3) : (15)

A) Convert the following

1)  $(26.25)_{10} = (?)_2$

2)  $(10111001.11101)_2 = (?)_{10}$

B) Convert the following

1)  $(3AC.8)_{16} = (?)_{10}$

2)  $(745.23)_8 = (?)_2$

C) Write a short note on OP- amp as a integrator.

D) i) Define Slew Rate & write its unit. ii) Define stability factor.

E) With the ckt diagram explain the use of op-amp as emitter coupled differential amplifier.

F) What is transistor biasing? What is its need?

\*\*\*\*\*