[Time: 3 Hours] [Marks: 80]

Please check whether you have got the right question paper.


N.B: 1. Question No 1. is compulsory.

- 2. Attempt **any three** from the rest.
- 3. Write neat and clean
- 4. Writing answer directly for numerical will not be considered for marks allotment
- 5. Assume any suitable data wherever required.
- Q.1 Answer any four

(20)

(10)

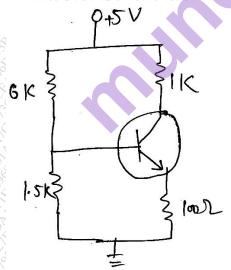
- a) Explain input and output characteristic of FET.
- b) Explain the ripple factor in case of center tapped full wave rectifier with C filter.
- c) Explain the Nyquist criteria of oscillation.
- d) Explain voltage shunt current feedback amplifier.
- e) Explain enhancement type MOSFET.
- Q.2 (a) Explain collpit oscillator with the help of suitable circuit diagram. Derive the expressing of (10) frequency for oscillation and necessary condition for oscillation.
 - (b) Explain double biased clipper with the help of suitable circuit and waveform.
- **Q.3** (a) For the given circuit find steady state DC parameters I_{cq} and V_{ceq} . Given $\beta = 100$ and $V_{be} = (10)$ 0.7v. Also state in which region the circuit in working.




(b) Derive the expressing for stabilization factors for voltage divider biased circuit of BJT. (10)

57809 Page **1** of **2**

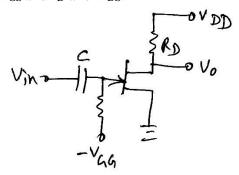- Q.4 (a) Draw the circuit diagram of cascade and cascade amplifiers and differentiate it. (10)
 - (b) Given $V_{GG}=1.5V$, $V_{DD}=15V$, $R_D=1.5k\Omega$, $R_G=1.5k\Omega$, $I_{DSS}=15mA$, $V_P=-4V$ Determine V_{GS} and I_D and V_{DS} .



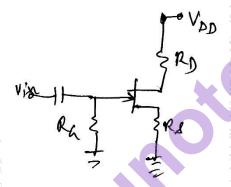(c) In JEET circuit show with self bias $V_{DD} = 25V$, $R_D = 3kW$, $R_S = 400W$, ID = 2.mA (05) Determine V_{DS} and V_{GS}



- Q.5 (a) Draw and explain the h-parameter model of BJT and derive the expression for A_v, A_i, R_i. (10) Consider CE configuration.
 - (b) Explain various configuration of feedback amplifier. Explain current series feedback in detail. (10)
- Q.6 Write short note on any two

(20)

(05)

- (a) Thermal runaway in BJT and FET
- (b) re model of BJT
- (c) RC phase shift oscillator.

57809 Page 2 of 2