

[3 Hours]

[Total Marks: 80]

Instructions:

1. Question No.1 is compulsory.
2. Attempt any three from the rest.
3. Figure to the right indicates full marks.
4. Assume suitable data if it is necessary.

- | | | |
|----------|---|----------------------------|
| 1 | a) Explain the need of biasing in BJT amplifiers.
b) Interpret the drain-source characteristics of n-channel depletion type MOSFET for $V_{GS} = 0V$ and $V_{GS} = -2V$.
c) Explain diode as positive shunt clipper.
d) Demonstrate the block diagram of op-amp with the function of each block. | (5 x 4) |
| 2 | a) Briefly discuss the different biasing techniques employed in BJT Amplifiers.
b) Draw the hybrid equivalent model of voltage divider bias CE amplifier and derive the expression for voltage gain. | (10)
(10) |
| 3 | a) Draw the small signal equivalent circuit of an n-channel MOSFET amplifier derive the expression of voltage gain.
b) Determine the values of I_{DQ} and V_{GSQ} for the Common Source n-channel Depletion type MOSFET in voltage divider bias configuration. $R_{G1} = 91M\Omega$, $R_{G2} = 15M\Omega$, $R_D = 6.8K\Omega$, $R_S = 3.3K\Omega$, $V_{DD} = 18V$, $I_{DSS} = 12mA$, $V_P = -3V$. | (10)
(10) |
| 4 | a) Explain op-amp as an inverting amplifier and design an inverting amplifier for voltage gain of -10.
b) Explain the working of astable multivibrator using IC 555. | (10)
(10) |
| 5 | a) Explain the construction and working of optoisolators.
b) Explain op-amp as voltage summing amplifier and derive the expression of output voltage. | (10)
(10) |
| 6 | Write short notes on ANY TWO
a) Monostable Multivibrator using IC555
b) Op-amp as Integrator
c) LM317 as Adjustable voltage Regulator | (20) |