

[3 Hours]

[Total Marks: 80]

**Instructions:**

1. Question No: 1 is compulsory.
2. Answer any three from the remaining five questions.

- |          |                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                       |                            |
|----------|---------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|----------------------------|
| <b>1</b> | <ol style="list-style-type: none"> <li>a) Recall the h-parameter equivalent model of Common Emitter voltage divider bias configuration and define all the h-parameters.</li> <li>b) Interpret the Drain-source characteristics of n-channel depletion type MOSFET with a neat figure for different values of <math>V_{GS}</math>.</li> <li>c) Draw the circuit diagram of op-amp based integrator circuit and write the expression of voltage gain.</li> <li>d) State the application of Opto-isolator with a neat figure.</li> </ol> | <b>(5 x 4)</b>             |
| <b>2</b> | <ol style="list-style-type: none"> <li>a) Discuss the need of biasing in BJT amplifiers. Illustrate the voltage divider biasing technique in detail.</li> <li>b) Draw the h-parameter equivalent model of a voltage divider bias Common emitter BJT amplifier and derive expression of voltage gain.</li> </ol>                                                                                                                                                                                                                       | <b>(10)</b><br><b>(10)</b> |
| <b>3</b> | <ol style="list-style-type: none"> <li>a) With a neat figure explain the construction and working principle of n-channel depletion type MOSFET.</li> <li>b) Illustrate the different biasing techniques employed in MOSFET amplifiers.</li> </ol>                                                                                                                                                                                                                                                                                     | <b>(10)</b><br><b>(10)</b> |
| <b>4</b> | <ol style="list-style-type: none"> <li>a) Explain op-amp as a non-inverting amplifier. Design a non-inverting amplifier for voltage gain of 11.</li> <li>b) Illustrate with neat diagram, the application of Op-amp as adder circuit. Derive the output expression.</li> </ol>                                                                                                                                                                                                                                                        | <b>(10)</b><br><b>(10)</b> |
| <b>5</b> | <ol style="list-style-type: none"> <li>a) Explain the construction and working of Schottky diode.</li> <li>b) Explain the block diagram of op-amp. Draw its frequency response characteristics.</li> </ol>                                                                                                                                                                                                                                                                                                                            | <b>(10)</b><br><b>(10)</b> |
| <b>6</b> | <p>Write short notes on <b>ANY TWO</b></p> <ol style="list-style-type: none"> <li>1) Astable Multivibrator using IC555</li> <li>2) Zener diode as clipper</li> <li>3) LM317 as Adjustable voltage Regulator</li> </ol>                                                                                                                                                                                                                                                                                                                | <b>(20)</b>                |