

(3 Hours)

[Total Marks: 80]

- N.B.:** (1) Question No. 1 is **compulsory**.  
 (2) Answer any **three** from the remaining **five** questions.  
 (3) **Assume** suitable **data** if necessary and justify the same.

1. Answer **any four**.

[20]

- (a) Define the terms oriented graph, tree and loop.  
 (b) Using Laplace transform, obtain the expression for current in impure inductor when a unit ramp signal is applied.  
 (c) Derive the condition for reciprocity in transmission parameters.  
 (d) State the various properties of LC driving point function.  
 (e) Using superposition theorem, find current  $I_x$  of network given in Fig.1

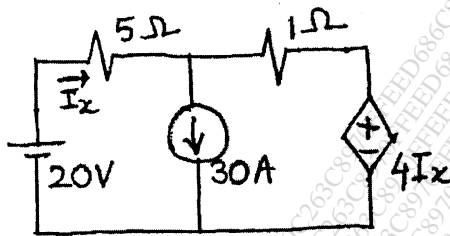


Fig. 1

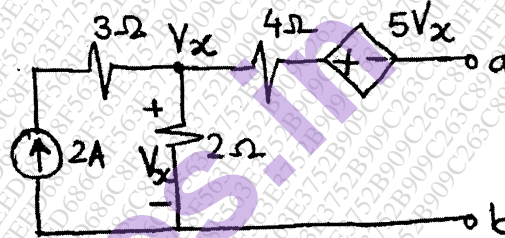


Fig. 2

Q2a Obtain Thevenin's equivalent of network shown in Fig. 2

[8]

Q2b For the graph shown in Fig. 3, write the tieset matrix and f-cutset matrix.

[8]

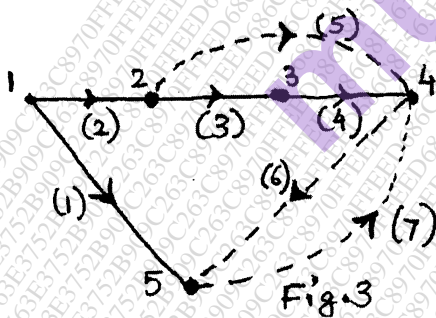


Fig. 3

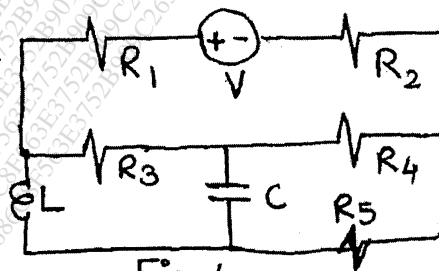



Fig. 4

Q2c Draw the dual of the network shown in Fig. 4


[4]

Q3a Explain the concept of super mesh and super node with an example. [5]

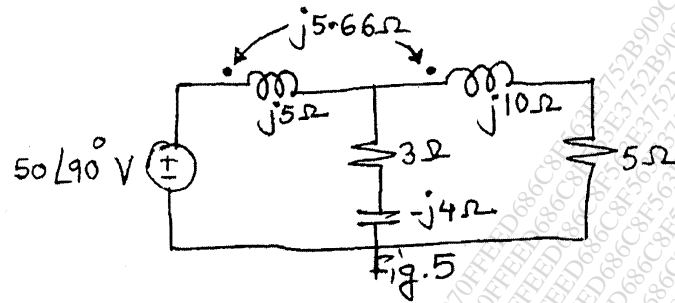Q3b Write the mesh equations for the circuit shown in Fig. 5 [5]




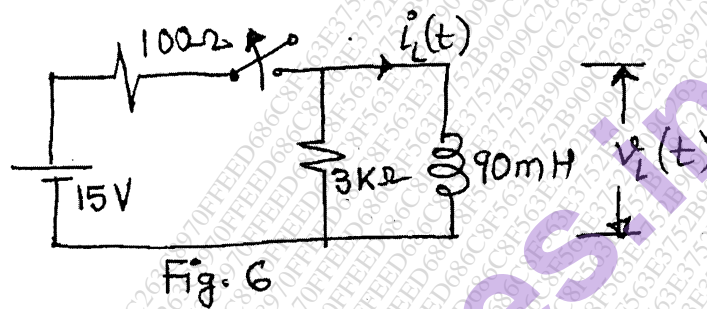
(c) For the network shown in Fig.6, steady state is reached with the switch closed. The switch is opened at  $t = 0$ . Obtain expressions for  $i_L(t)$  and  $v_L(t)$ . [10]



Q4a Using differential method, derive the expression for current in a series RL circuit. Draw its characteristics and define time constant. [6]



Q4b Mention the restrictions on pole and zero locations for driving - point functions. [4]

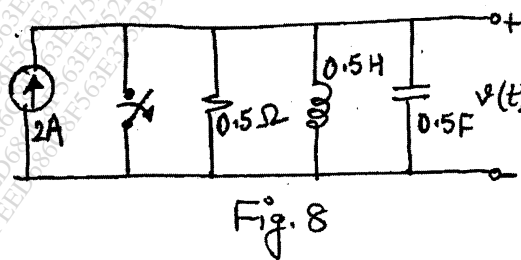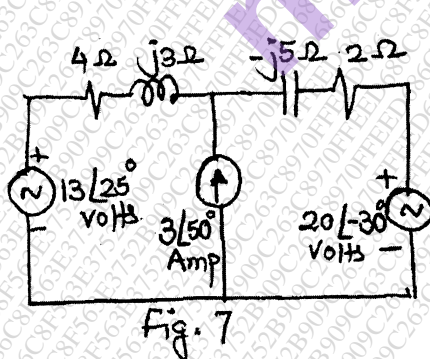Q4c Find the current  $I$  in the network shown in Fig.7, using superposition theorem [10]



Q5a The network shown in Fig.8 has acquired steady state at  $t < 0$  with the switch closed. The switch is opened at  $t = 0$ . Determine  $v(t)$ . [10]

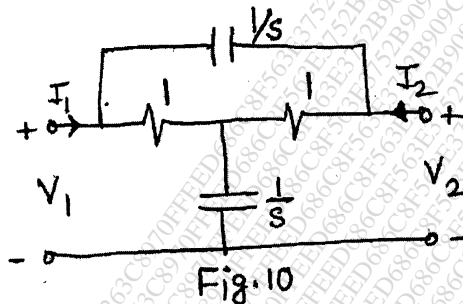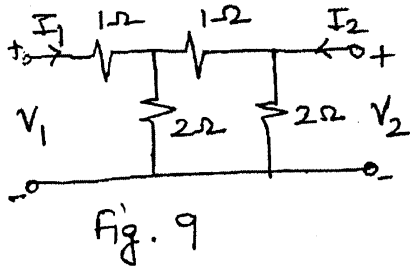Q5b For the network shown in Fig.9, find Z and h – parameters. [10]



Q6a Find the short circuit parameters for the network shown in Fig 10. [10]

Q6b The voltage  $V(s)$  of a network is given by  $V(s) = \frac{3s}{(s+2)(s^2+2s+2)}$ . Plot its pole – zero diagram and hence obtain  $v(t)$  using graphical method. [10]