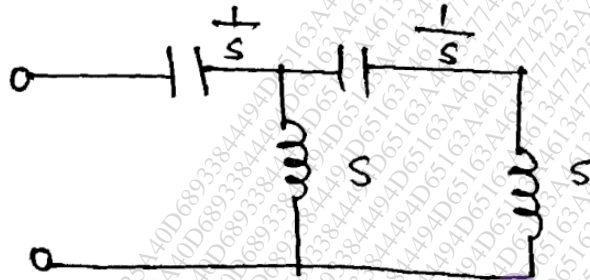



Please check whether you have the right question paper.

- N.B.:**
- 1) Questions No.1 is compulsory.
 - 2) Solve any three questions out of remaining five questions.
 - 3) Figures to the right indicate full marks.

1. a) State and explain properties of positive real function. (05)
 b) Compare series and parallel resonance circuit. (05)
 c) Determine the driving point impedance of the network shown. (05)




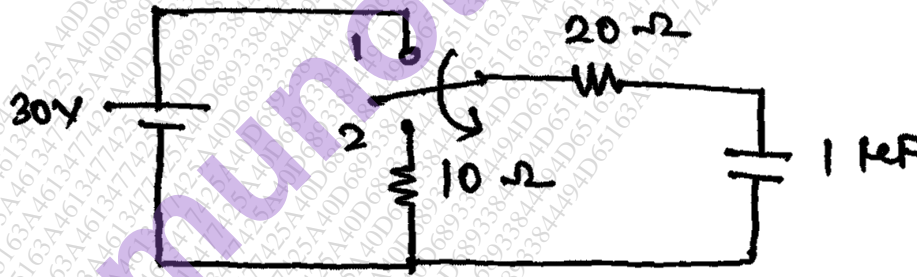- d) Determine whether $p(s) = s^4 + s^3 + 2s^2 + 3s + 2$ is Hurwitz. (05)
2. a) In the network shown the switch is changed from position 1 to 2 at $t = 0$. Find the values of i , $\frac{di}{dE}$ and $i, \frac{d^2i}{dt^2}$ at $t = 0^+$. (10)



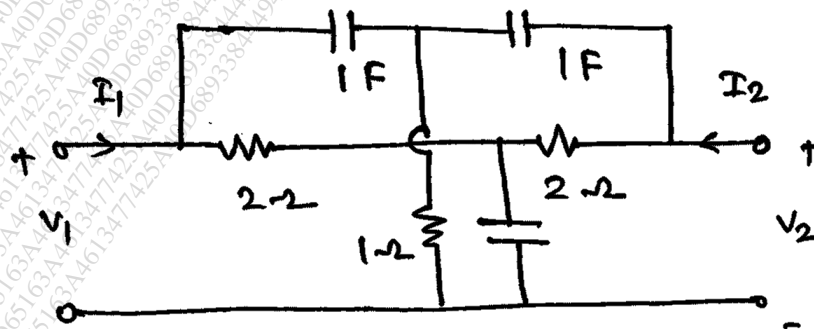
- b) Find the Foster forms of the following impedance function : (10)

$$z(s) = \frac{(s+1)(s+4)}{(s+5)(s+3)}$$
3. a) Find Y parameters for the network shown : (10)



TURN OVER

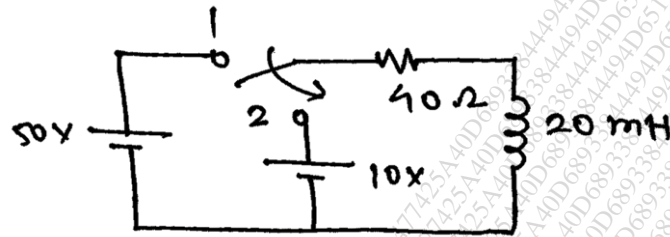- b) The network given below is under steady state with switch at position 1. At $t = 0$ the switch is moved to positions 2. Find $i(t)$. (10)




4. a) Test whether the following function is positive real : (05)


$$f(s) = \frac{s^2 + 6s + 5}{s^2 + 9s + 14}.$$

- b) Derive the condition for reciprocity and symmetry for the network in terms of z parameters. (10)
- c) Derive the relation for characteristic impedance of a transmission line. (05)

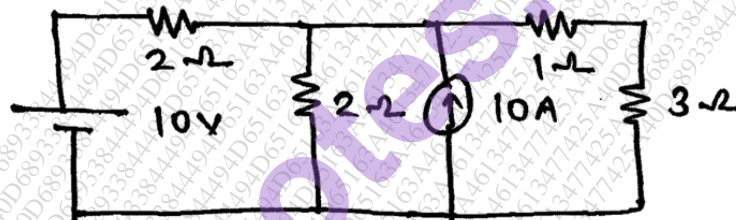
5. a) Find the current through 3Ω resistor using Thevenin's theorem : (05)



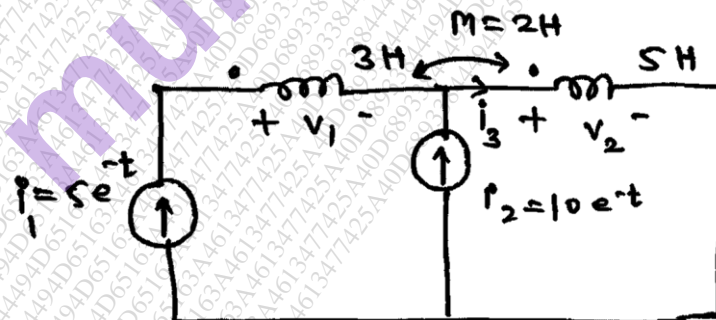- b) In the network shown find the voltages v_1 & v_2 : (05)



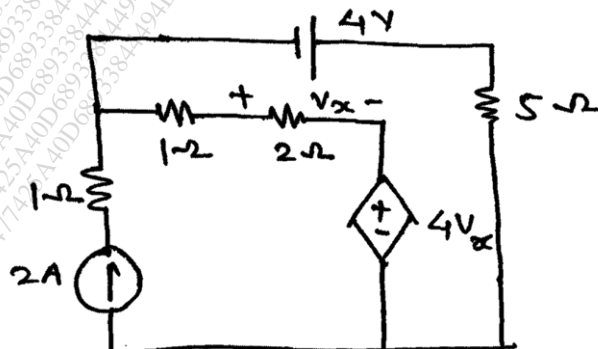- c) Find the current through 5Ω resistor for the network given below : (10)



TURN OVER

6. a) The characteristic impedance of a high frequency line is 100Ω . It is terminated in an impedance of $100 + j100 \Omega$. Using a smith chart find the impedance at $\frac{1}{8}$ wavelength away from the load end.
- b) In the network shown the switch is closed at $t = 0$ connecting a source e^{-t} to the network at $t = 0$. $V_c(0) = 0.5 \text{ V}$. Determine $V(t)$.

