

[Time: 3Hours]

[Marks:80]

Please check whether you have got the right question paper.

- N.B:**
1. Question no. 1 is compulsory.
 2. Attempt any three out of the remaining five questions.
 3. Use suitable data, wherever necessary

Q1 Attempt (any 4)

- Implement EX-OR gate using only NAND gates. **05**
- Explain FAN in, FAN out, power dissipation and noise immunity with reference to Digital IC's. **05**
- Explain glitch problem of ripple counter. **05**
- Write a note on VHDL Framework. **05**
- Draw the truth table and logic diagram of Full Subtractor.

Q2 A Draw a circuit diagram of two input TIL NAND gate and explain its operation. **10**

B Design 4 bit Johnson counter using J-K Flip Flop. Explain it operation using waveform. **10**

Q3 A Design a circuit with optimum utilization of PLA to implement the following functions. **10**

$$F1 = \sum m(0, 2, 5, 8, 9, 11)$$

$$F2 = \sum m(1, 3, 8, 10, 13, 15)$$

$$F3 = \sum m(0, 1, 5, 7, 9, 12, 14)$$

B Eliminate redundant states and draw reduced state diagram. **10**


PS	NS		O/P Y
	X=0	X=1	
A	B	C	1
B	D	F	1
C	F	E	0
D	B	G	1
E	F	C	0
F	E	D	0
G	F	G	0

Q4 A Implement the function using single IC 74151 and some gates. **10**

$$F = \sum m(1, 2, 4, 7, 10, 13, 14)$$

B Design asynchronous Mod-8 counter using T-Flip flop. **10**

 Q5 A Analyze the sequential state machine shown in figure. Obtain state diagram for the same.



B) Design a mod-16 up counter using IC 74163, draw the circuit diagram and explain its working.

Q6 Write notes on.

1. Stuck at '0' and Stuck at '1' faults.
2. XC 4000 FPGA Architecture
3. Master Slave JK Flip Flop
4. Mealy and Moore Sequential Machine