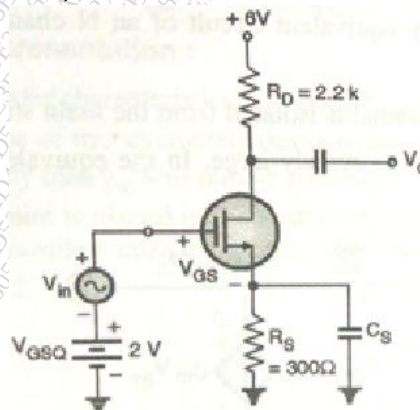


(3 Hours)

[Total Marks: 80]

- N.B:** (1) Question No.1 is compulsory.
 (2) Solves any three out of remaining question.
 (3) Assume suitable data if necessary.

- Q.1** Solve **any Four**
- Draw characteristics of PN junction in thermal equilibrium and explain. **05**
 - For a BJT amplifier, show with the help of a voltage divider bias circuit, how to draw A.C. load line? Draw graph. **05**
 - Explain the operation of MOSFET as amplifier. **05**
 - Explain construction, working principle and characteristics of Photodiode. **05**
 - Compare HWR, FWR and Bridge rectifier. **05**
- Q.2**
- Draw and explain positive and negative clamper circuit. **10**
 - Explain common base configuration of BJT as an Amplifier. **10**
- Q.3**
- Draw and explain VI and CV characteristics of P-channel enhancement type MOSFET with symbol. **10**
 - Explain operation and characteristics of Schottky diode. **10**
- Q.4**
- Explain the operation of fullwave rectifier and draw the output waveform for V_{Ldc} and I_{Ldc} . **10**
 - Explain working of BJT considering all possible current density components in an NPN transistor operation in active mode. **10**
- Q.5**
- Design single stage RC coupled amplifier to give a voltage gain of 80 with stability factor better than 11 and output voltage of 3 Vrms. Use NPN transistor with specifications $h_{fe} = 110-800$, $h_{ie} = 4.5 \text{ k}\Omega$, $V_{CE} = 45 \text{ V}$, $I_{C(max)} = 100 \text{ mA}$, $f_L = 300\text{Hz}$, $V_{CC} = 18\text{V}$. **15**
 - Draw small signal model of PN junction diode. What is the main use of this model? **05**
- Q.6**
- What is the small signal voltage gain of the MOSFET amplifier shown in diagram, if $V_T = 1 \text{ V}$, $K = 0.82\text{mA/V}^2$ and $\lambda = 0.022/\text{V}$. **10**



- Explain hybrid model of BJT. **10**

Deraile

Transistor type	P_{dmax} @ 25°C Watts	I_{cmx} @ 25°C Amps	V_{ce} volts d.c.
2N 3055	115.5	15.0	1-1
2N 3055	50.0	5.0	1-0
2N 149	30.0	4.0	1-0
2N 100	5.0	0.7	0-6
2N 147A	0.25	0.1	0-25
2N 525(PNP)	0.225	0.5	0-25
2N 147B	0.25	0.1	0-25

CBC 147A	2.7 K Ω	18 μ U	1.5 x
----------	----------------	------------	-------

2N 525 (PNP)	1.4 K Ω	25 μ U	3.2 $\times$
BC 147B	4.5 K Ω	30 μ U	2 $\times$
ECN 100	50 Ω	—	—
ECN 149	15 Ω	—	—
ECN 055	12 Ω	—	—
2N 3055	6 Ω	—	—

Type	$V_{DS} \text{ max.}$	V_{DS}
------	-----------------------	----------

Type	Volts	Volts
2N3822	50	50
BFW 11 (typical)	30	30