

**Time: 3 Hrs****Marks: 80****NB: (1) Question No. 1 is Compulsory.****(2) Attempt any three questions out of remaining five.****(3) Each question carries 20 marks and sub-question carry equal marks.****(4) Assume suitable data if required.**

Q.1 Answer any four

- a) Convert the decimal number (123)<sub>10</sub> to their octal, hexadecimal, BCD and gray code equivalent. 5M
- b) Explain characteristics of logic families. 5M
- c) Design and implement full adder circuit. 5M
- d) Write a short note on Hamming code. 5M
- e) Explain the working of a two –inputs CMOS NOR gate with neat diagram 5M
- f) Explain the structural VHDL description of 2 to 4 decoder in detail. 5M

Q.2 a) Draw the circuit diagram of TTL NAND gate with totem pole output and explain its working with the help of a truth table. 10M

Q.2 b) Design and implement the following expression using a single 8:1 multiplexer

$$F(A,B,C,D) = \sum m(0,1,3,4,8,9,15).$$
 10M

Q.3 a) Design and implement D FF using JK FF and T FF using SR FF 10M

Q.3 b) Explain the working of 3 bit asynchronous counter with proper timing diagram 10M

Q.4 a) What is shift register? Explain any one type of shift register. Give its application. 10M

Q.4 b) Reduce the following state table using partitioning method of state reduction. 10M

PS	Next State		Output	
	X=0	X=1	X=0	X=1
S0	S1	S2	0	0
S1	S3	S4	0	0
S2	S5	S6	0	0
S3	S0	S0	0	0
S4	S0	S0	1	0
S5	S0	S0	0	0
S6	S0	S0	1	0

Q.5 a) Implement following function using PLA. 10M

$$F1 = \sum m = (0,1,3,4) \text{ and } F2 = \sum m = (1,2,3,4,5)$$

Q.5 b) Design 2 bit comparator and implement using logic gates. 10M

Q.6 a) Implement and explain 4 bit BCD adder using IC 7483 10M

Q.6 b) Write a Verilog code for 8:1 multiplexer using data flow modelling. 10M