

**Three Hours****80 Marks**

- N.B.
- 1) **Question-1** is compulsory.
  - 2) Solve any **Three** questions from the remaining.
  - 3) Assume suitable data wherever necessary.
  - 4) All questions carry equal marks.

Q.1 Solve any **four** of the following:

**20**

- a) Explain cross over distortion in Class B power amplifier.
- b) Explain Darlington pair amplifier.
- c) Explain Gunn diode.
- d) Explain high frequency equivalent circuit of MOSFET.
- e) Draw MOSFET differential amplifier with active load.

Q.2 a) Explain working of TRIAC with construction and V-I characteristics. Also give its applications.

**10**


b) Explain voltage series and current shunt feedback amplifiers.

**10**

Q.3 a) Calculate lower cut off frequency of the following circuit.

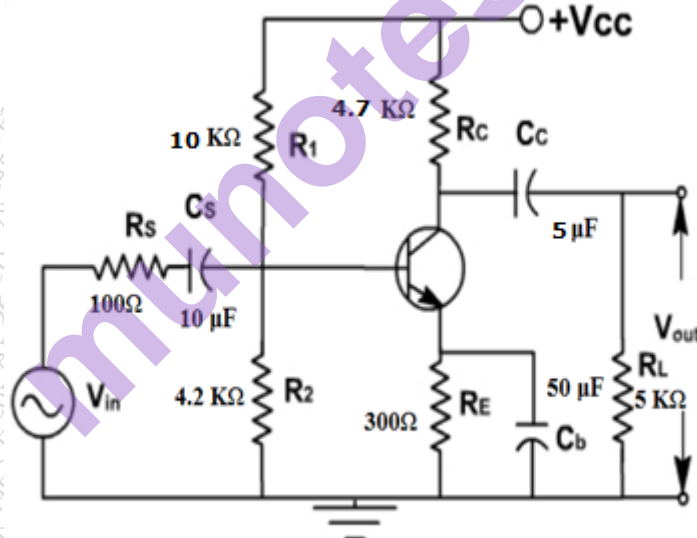**10**

$$\beta=100, r_{\pi}=1.5\text{K}\Omega, g_{m2}=50\mu\text{A/V}, C_{\pi}=15\text{pF}, C_{\mu}=1\text{pF}$$



b) Explain UJT as a relaxation oscillator with neat circuit diagram.

**10**

Q.4 a) Explain Class A power amplifier with circuit diagram and derive equation for efficiency.

**10**


b) Explain small signal analysis for MOSFET active load circuit.

**10**

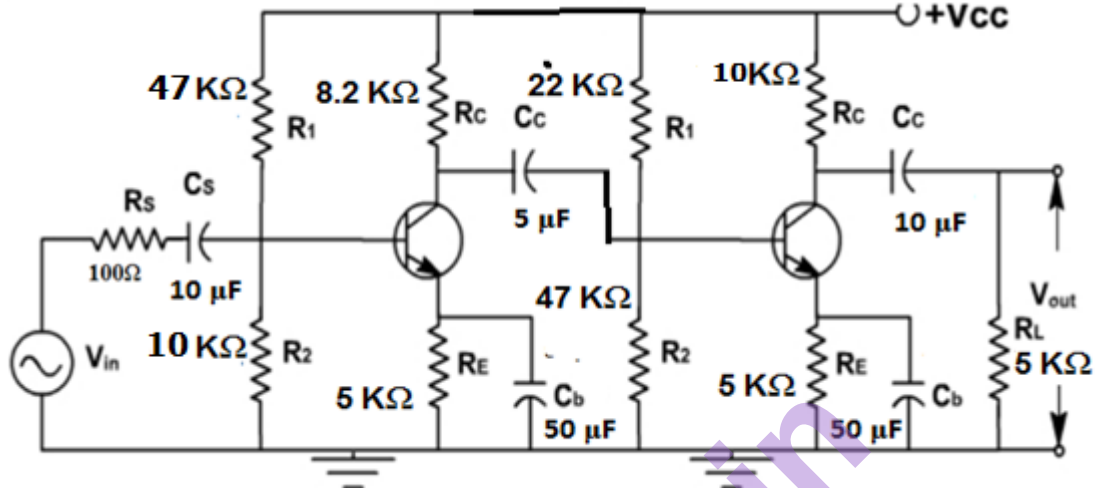Q.5 a) Calculate bandwidth for two stages RC coupled CE amplifier shown in the circuit below: **10**

$$\beta_1 = \beta_2 = 100, r_{\pi 1} = r_{\pi 2} = 1.5 \text{ K}\Omega, g_{m1} = g_{m2} = 50 \text{ mA/V}$$

$$C_{\pi 1} = C_{\pi 2} = 10 \text{ pF}, C_{\mu 1} = C_{\mu 2} = 5 \text{ pF}$$



b) Explain Hartley oscillator. Design the same for 5MHz.

**10**

Q.6 Write short notes on any **three** of the following:

**20**

- SCR
- Wein bridge oscillator.
- Cascode BJT amplifier
- Class B push pull power amplifier

\*\*\*\*\*