

(3 Hours)

Total Marks: 80

N.B: (1) Question No.1 is compulsory and solves ant three questions from remaining questions.  
(2) Assume suitable data if necessary.  
(3) Draw neat and clean figures.

1. Answer any four:
  - (a) Explain trade off in Analog design with the help of analog design octagon 5
  - (b) For N channel MOSFET draw i) small signal model ii)small signal model with channel length modulation iii)small signal model with body effect 5
  - (c) Explain importance of Miller theorem 5
  - (d) Explain input output characteristic of Phase detector circuit 5
  - (e) Compared performance of op-amp topologies 5
2.
  - (a) Derive voltage gain of diode connected load CS amplifier 10
  - (b) Derive equation of differential gain, common mode gain, CMRR of differential amplifier 10
3.
  - (a) Explain in detail how to generate temperature independent reference 10
  - (b) Explain concept of switched capacitor circuit and explain switched capacitor amplifier in detail. 10
4. (a) Design an amplifier that meet the following specification with a phase margin of 60.assume the channel length is to be  $1\mu\text{m}$   
 $A_v > 5000\text{v/v}$ ,  $V_{dd} = 2.5$ ,  $V_{ss} = -2.5\text{v}$ ,  $GB = 5\text{MHz}$ ,  $CL = 10\text{pf}$ ,  
 $SR > 10\text{v}/\mu\text{sec}$ ,  $V_{out} \text{ range} = \pm 2\text{V}$ ,  $ICMR = -1 \text{ to } 2\text{V}$ ,  $P_{diss} \leq 2\text{mw}$ . 20
5.
  - (a) List down the performance parameter of VCO and explain trade off between them 10
  - (b) Give comparison of full custom design and semi custom design 10
6. Write short notes( any three) 20
  - (a) White and flicker noise in MOSFET
  - (b) AMS design flow
  - (c) Clock feed through in MOSFET
  - (d) Band gap reference

\*\*\*\*\*