

Duration: 3hrs

Max. Marks:80

NB:

- (1) Question No.1 is compulsory.
- (2) Answer any **three** from remaining questions.
- (3) **Figures** to the right indicate full marks.
- (4) Assume suitable data if required.

Q.1 Attempt **any four**

- | | |
|---|----------|
| a Compare JFET and MOSFET | 5 |
| b Explain the Significance of stability factor | 5 |
| c Why crystal oscillator is most stable oscillator? | 5 |
| d Describe thermal runaway in BJT | 5 |
| e What is clipping and clamping explain with one example. | 5 |

Q.2

- | | |
|--|-----------|
| a Draw BJT CE amplifier with any biasing circuit and derive expression for voltage gain, input impedance and output impedance. | 10 |
| b What is Varactor diode? Explain construction and operation of varactor diode. | 10 |

Q.3

- | | |
|--|-----------|
| a Sketch the circuit of Wein Bridge Oscillator using BJT and derive an expression for the frequency of oscillation. | 10 |
| b For Common source amplifier with N-channel EOMOSFET determine A_v , Z_i , and Z_o . $V_{DD}=21V, R_1=42K, R_2=33K, R_D=5K, R_S=1.5K$. The MOSFET parameters are: $V_{TN}=1.5V, K_n=0.5mA/V^2$ | 10 |

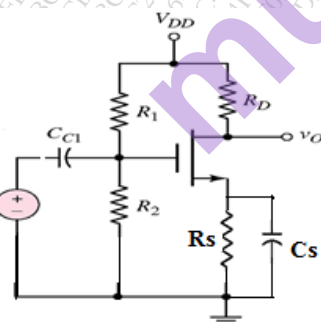


Fig.2

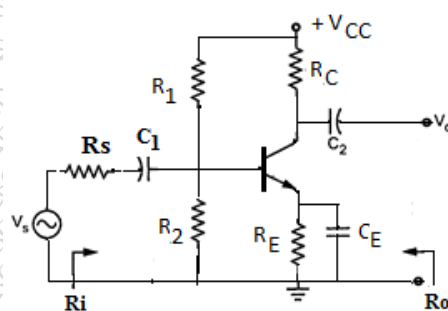


Fig.3

Q.4 For the amplifier shown in Fig.3 analyze and determine. Derive the expression for small- **10**

- | | |
|---|-----------|
| a signal voltage gain, input and output impedance. BJT and circuit parameters are: $\beta=100, V_{BE}=0.7V, V_A=100V, R_1=93.7K, R_2=6.3k, R_C=6K, R_S=0.5K, V_{CC}=12V$. | 10 |
| b Draw the constructional diagram of N-Channel JFET, and explain the operation and thus obtain the V-I characteristics. | 10 |

Q.5

- a An N-Channel FET with common drain amplifier shown in fig.4 has the following parameters: $I_{DSS}=10\text{mA}$, at $V_P=-4\text{V}$. Determine Small signal voltage gain, input impedance and output impedance. If $R_1=10\text{M}$, $R_2=2\text{M}$, $V_{DD}=18\text{V}$, $R_S=1.2\text{k}$, $R_L=10\text{K}$. 10

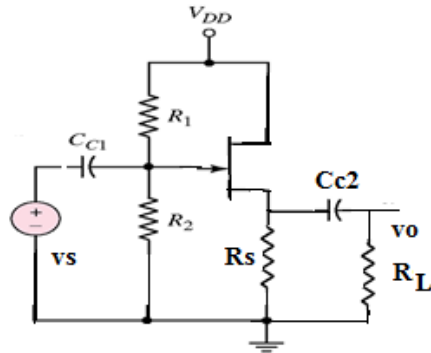


Fig.4

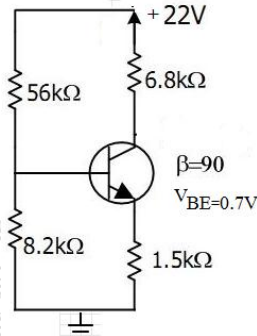


Fig.5

- b For the circuit shown in figure 5. Determine Q point co-ordinates. 10

Q.6

Attempt the following

- LC oscillator and its application. 5
- Small signal h- parameter parameters of BJT 5
- Depletion MOSFET operation. 5
- Compare BJT and FET 5
