

Time: 3 Hours

Max. Marks: 80

Q1 is compulsory. Attempt any three from Q2 to Q6.

**Q1****Solve any Four****5 marks each**

- A Explain the operation of a semiconductor pn junction diode with the help of VI characteristics.
- B Explain Miller's capacitance theorem.
- C Compare BJT CE amplifier and JFET CS amplifier.
- D What is crossover distortion in Class B power amplifiers?
- E Let  $V_{DD} = 5V$ ,  $V_{t,1} = 1V$ ,  $k_{n,1}' = 20\mu A/V^2$  and  $R = 1K\Omega$ . What should be  $(W/L)_1$  needed for creating  $I_{ref} = 1mA$ ? What should be  $(W/L)_2$  if  $I_o = 7mA$ ? Refer Fig. 1

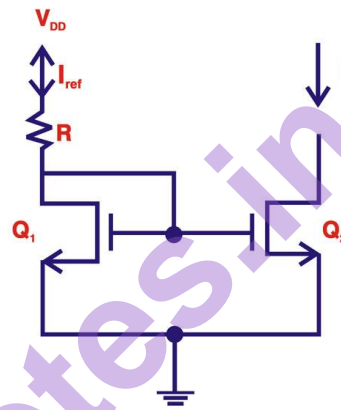


Fig. 1

**Q2****10 marks each**

- A Design a feedback bias circuit for n-channel E-MOSFET with operating drain current of 0.5 mA. Given:  $V_{DD} = 5V$ ,  $k_n' = 100\mu A/V^2$ ,  $W = 1.8\mu m$ ,  $L = 180nm$ ,  $V_{T0n} = 1V$ . Use a standard resistor value for  $R_D$  and recalculate  $I_D$  and  $V_D$ . Refer fig. 2.

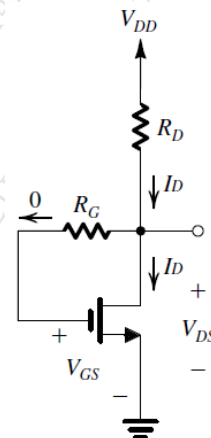


Fig. 2

- B Draw a small signal equivalent circuit of an E-MOSFET CS amplifier given in fig. 3 and derive the expression for voltage gain, input resistance and output resistance.

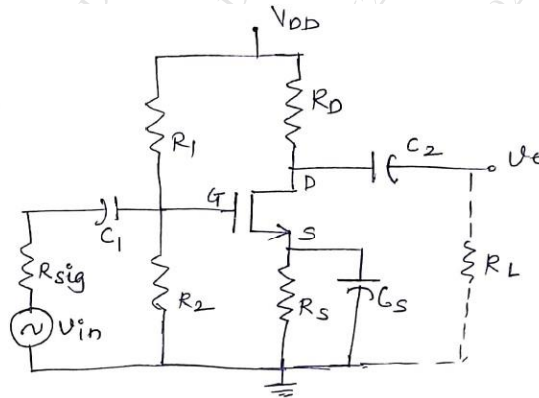


Fig. 3

Q3

- A  
B  
C

Explain construction and working of n-channel E-MOSFET

5 marks

What is thermal runaway and how it can be avoided?

5 marks

Calculate low cutoff frequencies due to coupling and bypass capacitors of the circuit given in fig. 4

10 marks

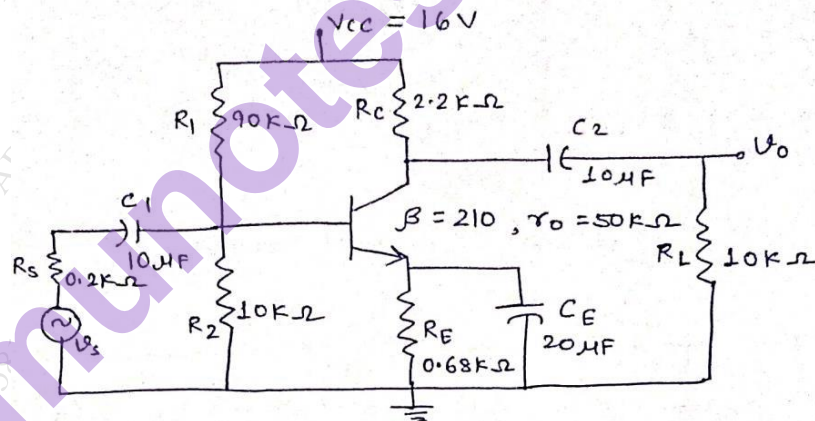


Fig. 4

Q4

- A

Determine  $f_{\beta}$  and  $f_T$  for the given circuit. Assume  $I_E = 1.65$  mA. Refer Fig.

5

5 marks

$$R_S = 1 \text{ k}\Omega, R_1 = 40 \text{ k}\Omega, R_2 = 10 \text{ k}\Omega, R_E = 2 \text{ k}\Omega, R_C = 4 \text{ k}\Omega, R_L = 2.2 \text{ k}\Omega$$

$$C_S = 10 \text{ }\mu\text{F}, C_C = 1 \text{ }\mu\text{F}, C_E = 20 \text{ }\mu\text{F}$$

$$h_{fe} = 100, r_o = \infty \text{ }\Omega, V_{CC} = 20 \text{ V}$$

$$C_{\pi}(C_{be}) = 36 \text{ pF}, C_{\mu}(C_{bc}) = 4 \text{ pF}, C_{ce} = 1 \text{ pF}, C_{W_i} = 6 \text{ pF}, C_{W_o} = 8 \text{ pF}$$

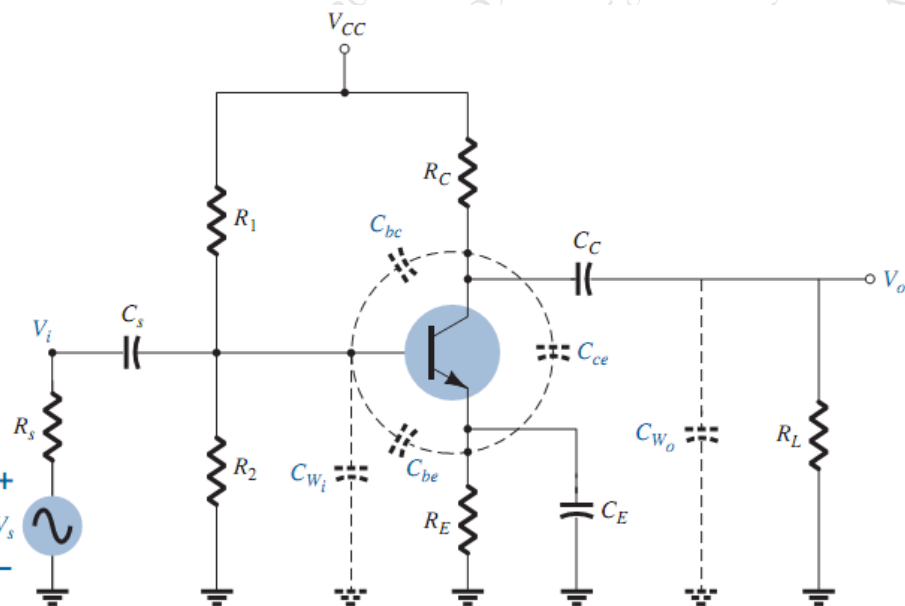


Fig. 5

B Draw and explain high frequency model for BJT in CE configuration.

5 marks

C Draw and explain a series fed class A power amplifier with the help of neat diagram and waveforms and derive the expression of power efficiency.

10 Marks

Q5  
A

Design a voltage divider bias circuit to operate at the given conditions.

Calculate the stability factors  $S(I_{CO})$ ,  $S(V_{BE})$ ,  $S(\beta)$ . Refer Fig. 6 10 Marks

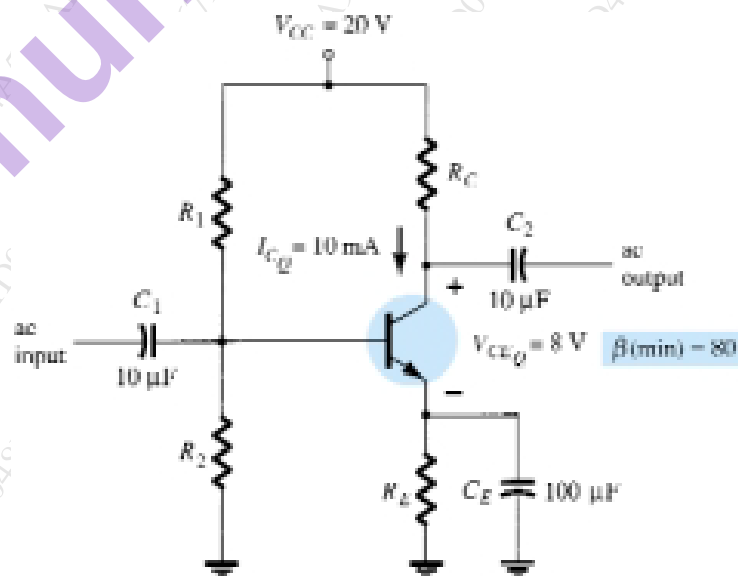


Fig. 6

B Determine the input impedance, output impedance, voltage gain and current gain for the given circuit. Refer fig. 7

10 Marks

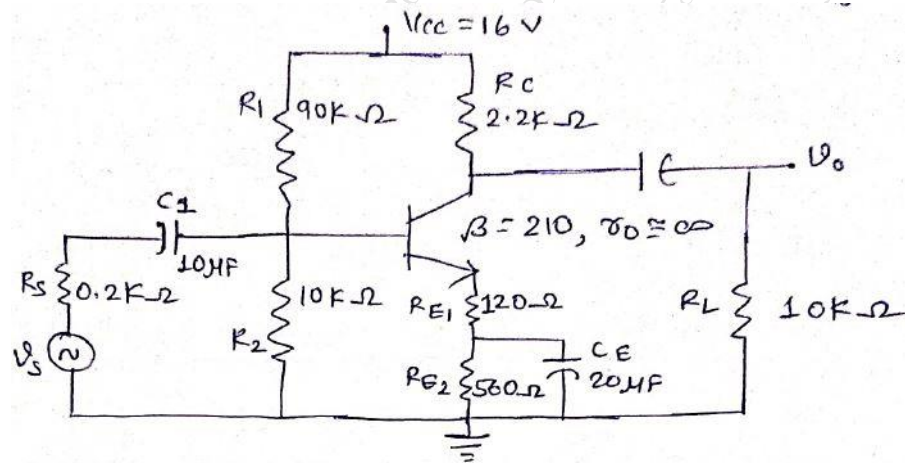


Fig. 7

## Q6

- A Derive the equation of CMRR for the MOS differential pair amplifier. **10 Marks**
- B Write short note on:
- E-MOSFET as a differential amplifier **5 Marks**
  - Zener diode as a voltage regulator **5 Marks**