

Time: 3 Hours


Total Marks: 80

N.B.

- 1) Question No. 1 is Compulsory
- 2) Out of remaining questions, attempt any three
- 3) Assume suitable data if required
- 4) Figures to the right indicate full marks


1 (A) Draw equivalent circuit for given magnetically coupled circuit.

05

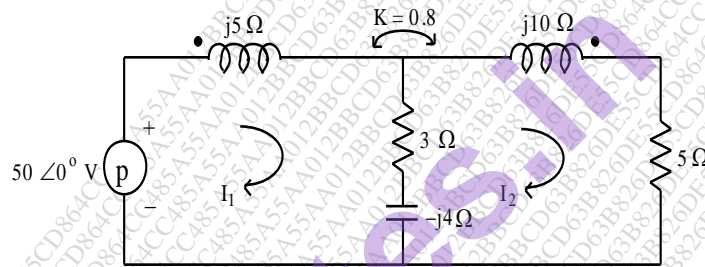

(B) In the network shown in Fig., at $t = 0$, switch is opened. Calculate v , $\frac{dv}{dt}$ at $t = 0+$.

05

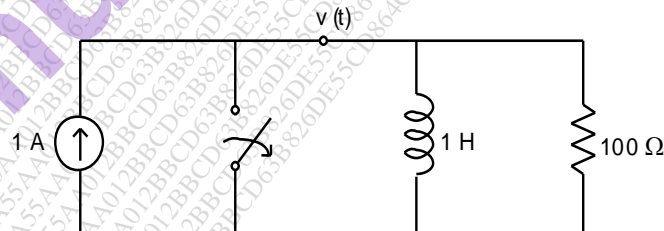


(C) The Z parameters of a 2 port network are, $Z_{11} = 20\ \Omega$, $Z_{22} = 30\ \Omega$, $Z_{12} = Z_{21} = 10\ \Omega$. Find Y parameters.

05

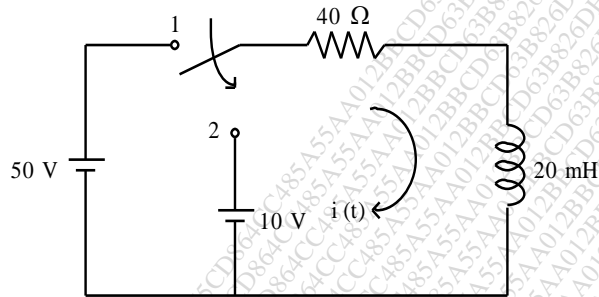
(D) Two two port networks are connected in parallel. Prove that the sum of the corresponding individual parameters is equal to the overall y parameters.

05


- 2 (A) The network of Fig. is under steady state with switch at position 1. At $t = 0$, switch is moved to position 2. Find $i(t)$. 10



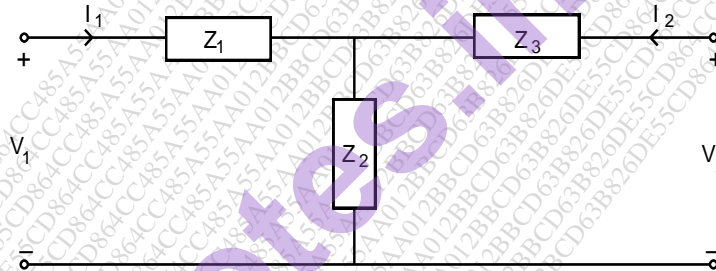- (B) The Z-parameters of a two port are : $Z_{11} = 20 \Omega$, $Z_{12} = Z_{21} = 10 \Omega$, $Z_{22} = 30 \Omega$. Find equivalent T-network. 10



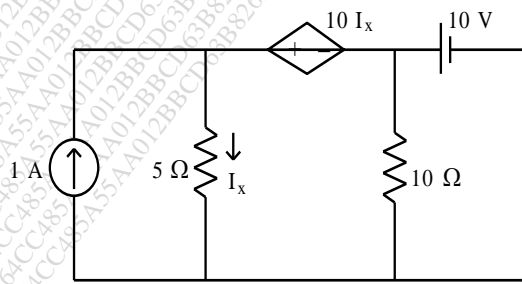- 3 (A) Determine Thevenin's equivalent network for the Fig. shown. 10



- (B) The parameters of a transmission lines are $R = 65 \Omega/\text{km}$, $L = 1.6 \text{ mH}/\text{km}$, $G = 2.25 \text{ mmho}/\text{km}$, $C = 0.1 \mu\text{F}/\text{km}$. Find
i) Characteristic Impedance 10

- ii) Propagation Constant
- iii) Attenuation Constant
- iv) Phase Constant at 1 kHz

4 (A) Determine whether following functions are positive real


10

i) $\frac{s^4 + 2s^3 + 3s^2 + 1}{s^4 + s^3 + 3s^2 + 2s + 1}$

ii) $\frac{s^2 + 2s}{s^2 + 1}$


(B) In the network of Fig. find V_0 .

10

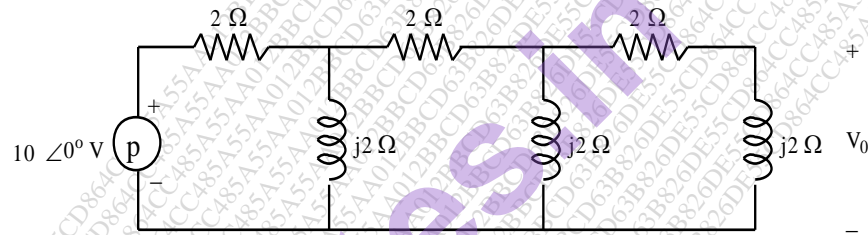

5 (A) Find Y-parameters for the network shown in Fig

10

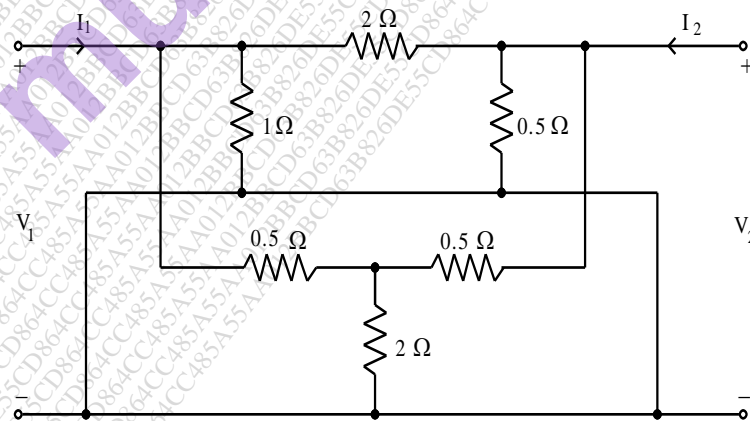

(B) Realize the following functions in Foster I and Foster II form

10

$$F(s) = \frac{4(s+1)(s+3)}{(s+2)(s+6)}$$

- 6 (A) A transmission line has a characteristics impedance of 50 ohm and terminate in a load $Z_L = 25 + j50$ ohm. Use smith chart and Find VSWR and Reflection coefficient at the load. **10**
- (B) The switch in Fig. is open for a long time and closes at $t = 0$. Determine $i(t)$ for $t > 0$. **10**

