

(3 Hours)

[Total Marks: 80]

- N.B.: (1) Question No. 1 is **compulsory**.  
 (2) Solve any **three** questions from the remaining **five**  
 (3) **Figures** to the **right** indicate **full** marks  
 (4) Assume suitable data if necessary and mention the same in answer sheet.

- Q.1** Attempt **any 4** questions
- (a) What is the need of negative feedback in op-amp based circuit? [05]
  - (b) What is input offset voltage and output offset voltage of an op-amp? [05]  
How to measure it practically?
  - (c) With the help of a neat circuit diagram explain the working of Multiplier 534. [05]
  - (d) Give the working principle of switching regulator. [05]
  - (e) Draw mod-10 ripple counter using IC 7490. [05]
- Q.2**
- (a) Draw the circuit diagram of a square and triangular waveform generator using op-amps and explain its working with the help of waveforms. For variation in duty cycle what is the modification needed in the circuit. [10]
  - (b) Explain IC 555 as astable multivibrator and hence design an astable multivibrator using IC 555 to obtain 50% duty cycle. [10]
- Q.3**
- (a) Design a second order Butterworth high pass filter for cut off frequency of 1 kHz and pass-band gain of  $AF=2$ . [10]
  - (b) With the help of a neat circuit diagram explain the working of IC 74163 synchronous 4 bit binary counter. [10]
- Q.4**
- (a) Design a voltage regulator using IC 723 to give output voltage  $V_o = 5\text{ V}$  to  $15\text{ V}$  and output current of  $2\text{ A}$ . [10]
  - (b) With a neat circuit explain the working of window detector using op-amp. Give its application. [10]
- Q.5**
- (a) Draw a neat circuit diagram of RC phase shift oscillator using op-amp. Derive its frequency of oscillation. What are the values of  $R$  and  $C$  if its frequency of oscillation is  $2\text{ kHz}$ ? [10]
  - (b) Draw a mod-10 counter using IC 7493. Draw its timing diagram. [10]
- Q.6** Write a note on: (**Attempt any two**)
- a) Instrumentation amplifier. [10]
  - b) Full wave precision rectifier. [10]
  - c) 74181 ALU. [10]

\*\*\*\*\*