

(3 Hours)

[Total Marks: 80]

N.B.: (1) Question No. 1 is **compulsory**.

(2) Solve any **three** questions out of remaining **five**.

(3) Figures to **right** indicate **full** marks.

(4) Assume suitable **data** where **necessary**.

- Q1. Solve **any four** 20
- Prove that NAND and NOR gate are universal gate.
 - Convert following decimal number to Binary, Octal, Hexadecimal and Gray code
i) $(256)_{10}$ ii) $(45)_{10}$
 - Draw and explain circuit diagram of a differentiator using Op-amp.
 - Covert S-R flip flop to D flip flop.
 - Derive the relation between α and β
- Q2. 10
- Explain Voltage Divider Biasing Circuit with its stability factor.
 - Implement following using only one 8:1 Multiplexer and few gates.
 $F(A,B,C,D) = \sum m(0,1,2,3,5,7,9,11,12,15)$ 10
- Q3. 10
- Draw circuit diagram and explain the operation of Astable Multivibrator using IC555. 10
 - Design 4-bit binary to Excess-3 code conversion. 10
- Q4. 10
- Minimize the following four variable logic function using K-map and design by using only NAND gates
 $f(A,B,C,D) = \sum m(0,1,2,3,4,7,8,9,11,12,15)$ 10
 - What are the different methods used to improve CMRR in Differential Amplifier. Explain one in brief. 10
- Q5. 10
- Design a Mod 12 asynchronous counter using J-K-Flip Flop. 10
 - With the help of neat diagram explain functioning of Universal Shift register. 10
- Q6 Write short notes on **any four** 20
- Design XOR gate using only NOR gates.
 - Explain working of a Current Mirror Circuit.
 - Write VHDL program for half adder.
 - Explain Encode and Decoder.
 - Explain working of Zener diode with VI characteristics.
