

EP803 - Advanced Electrical Drives

P. Pages : 2

Time : Three Hours

**GUG/W/16/7052**

Max. Marks : 80

- Notes :
1. All questions carry equal marks.
 2. Assume suitable data wherever necessary.
 3. Illustrate your answers wherever necessary with the help of neat sketches.
 4. Use of Non – Programmable calculators is permitted.
 5. Student must have to solve the questions as per internal choice.

1. a) In the motor load system, motor and load torques are given by, **6**

$$T = 1 + 2 w_m \text{ and } T_L = 3\sqrt{w_m}$$
 obtain the equilibrium points and determine their steady state stability.
- b) Draw the block diagram of typical electrical drive system and explain the function of power modulator as a converter. **6**
- c) Explain four quadrant operation of electric drives. **4**

OR

2. a) Explain stability of electrical drives & derive its necessary condition. **8**
- b) Derive the equations for equivalent torque and equivalent moment of inertia referred to the motor shaft for a typical drive system, with two different loads of which one has the rotational motion connected directly to the motor shaft & another with translational motion connected through gears. **8**
3. a) Explain the working of single phase fully controlled, rectifier fed, separately excited DC motor drives with relevant wave forms. Also obtain the equations to represent speed – torque characteristics. **9**
- b) A 220 V, 1500 rpm, 10 Amp sep. Excited DC motor is fed from single phase fully controlled rectifier with an ac source voltage of 230 V, 50Hz, $R_a = 2\Omega$, Conduction can be assumed to be continuous. Calculate firing angles for **7**
 - i) Half the rated motor torque and 500 rpm
 - ii) Rated motor torque and (-1000) rpm.

OR

4. a) What are the various breaking methods of DC Drives? Compare dynamic and regenerative breaking. **6**
- b) Draw the drive circuit for two quadrant chopper. Explain its working with armature current & voltage waveforms fed to DC motor. **6**
- c) Write short note on control of fractional hp motors. **4**

5. a) Explain the working principle of V/f method of speed control of induction motor with the help of speed – torque characteristics showing all speed ranges for below and above base value. 6
- b) Compare stepped wave and PWM inverter fed induction motor drives. 4
- c) How can you obtain variation in rotor circuit resistance using static control? Draw drive circuit. 6

OR

6. a) What do you mean by slip power? Explain any one method in detail of utilizing this power for control drive. 8
- b) Draw a neat diagram of 3 phase current source inverter fed induction motor drive. Explain the working in detail. 8
7. a) With the help of diagram explain the working of reversing cold rolling mill. 8
- b) Explain with reason the type of electrical drives that will be used for following industries
i) Cement mill ii) Paper mill 8

OR

8. a) Explain with neat diagram the working of automatic slip regulator. Give its area of application. 8
- b) What are the various sections associated with paper industry? How this process are carried out. 8
9. a) With the help of block diagram explain true synchronous mode of variable frequency synchronous motor drives. What are its main features? 8
- b) A 1000 KW, three phase 6.6 KV, 50Hz, 6 pole, unity power factor, star connected synchronous motor has following parameters $X_s = 30\Omega$, $R_s = 0$. Motor is connected by line commutated and load commuted converters in self control mode. The load side converter operates at fixed firing angle of 0° . When working as a rectifier and fixed firing angle of 150° when working as an inverter. Calculate the source side converter firing angle for following cases. 8
- i) Motor is operating at rated torque & 750 rpm.
- ii) Motor is generating at torque equal to the rated torque & 750 rpm.
- Assume that the motor operates at a constant V/f ratio, and neglect commutation overlap.
- 3 - ϕ ac source voltage is 6.6 KV. The dc link inductor resistance of 0.2Ω .

OR

10. a) With the help of equivalent circuit derive expression for steady state torque for the cylindrical rotor synchronous motor. 5
- b) Write brief note on synchronous motor drive using cycloconverter. 5
- c) Describe the operation of brushless dc motor and explain its advantages over unipolar drives. 6
