

M.Sc. (Physics) (CBCS Pattern) First Semester
PSCPHYT03 - Core-III - Electronics Paper-III

P. Pages : 2

Time : Three Hours



GUG/W/18/11181

Max. Marks : 80

-
- 1. EITHER:-**
- a) Explain construction and working of P-channel JFET. **8**
- b) Discuss in details Schottky diode and Tunnel diode. **8**
- OR**
- e) Write a short note on: **8**
- i) Photo-diode
- ii) Solar cell
- f) Discuss in detail silicon controlled rectifier (SCR). **8**
- 2. EITHER:-**
- a) Explain in detail working of MOSFET as an amplifier. **8**
- b) Explain construction and working of Zener regulated power supply. **4**
- c) Explain in short working of RC coupled amplifier. **4**
- OR**
- e) Write a short note on: **8**
- i) Phase shift Oscillator.
- ii) Hartley Oscillator.
- f) Explain construction and working of clipping and clamping circuit. **8**
- 3. EITHER:-**
- a) Explain construction and working of Astable and monostable multi-vibrator using suitable time diagram. **8**
- b) Explain working of OPAMP as a adder, integrator and differentiator. **8**
- OR**
- e) Explain construction and working of sweep generator using SCR. **8**
- f) Construct AND, OR, NOT and NOR by using NAND gates and NOR gates. **8**

4. EITHER:-
- a) Explain digital pulse code modulation (PCM.). 8
 - b) Discuss in detail, fundamentals of optical communication. 8

OR

- e) Explain working of magnetron and Gunn diode oscillator. 8
 - f) Explain working of cavity resonator. 8
5. Attempt all the followings.
- a) Write short note on LCD. 4
 - b) Explain need of feedback in amplifier. 4
 - c) Explain working of operation amplifier as a comparator. 4
 - d) Discuss demodulation. 4
