

Network Analysis / Network Theory

P. Pages : 4

Time : Three Hours



GUG/W/18/11487

Max. Marks : 80

- Notes :
1. All questions carry equal marks.
 2. Assume suitable data wherever necessary.
 3. Illustrate your answers wherever necessary with the help of neat sketches.
 4. Use of non-programmable electronic calculator is permitted.

1. a) In the network of fig. Q. 1, Find the value of source voltage V_1 , which results in zero current through $j5\Omega$ reactance use mesh analysis. 8

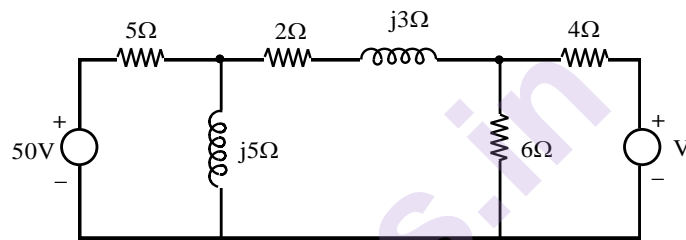


Fig. Q. 1

- b) In the network of Fig. Q. 1, find the value of source voltage V_1 , which results in current of 1A through $j5\Omega$ reactance. Use nodal analysis. 8

OR

2. a) In the network of Fig. Q. 2(a), find the value of current through 4Ω resistance using mesh analysis. 8

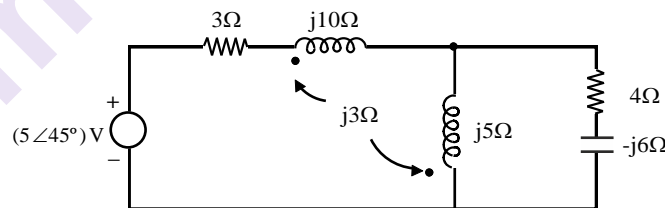


Fig. Q. 2 (a)

- b) Using nodal analysis, find the value of current through 3Ω resistance in the network of fig. Q. 2(b). 8

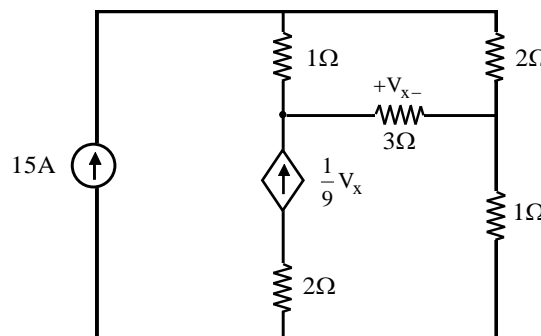


Fig. Q. 2 (b)

3. a) In the network of fig. Q.3 (a), find the value of current through 2Ω resistance using superposition theorem. 6

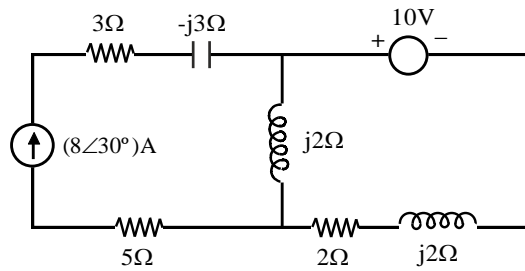


Fig. Q. 3 (a)

- b) In the network of fig. Q.3(b), find the value of resistance R , which will draw maximum power from the network. Also find the value of maximum power. 10

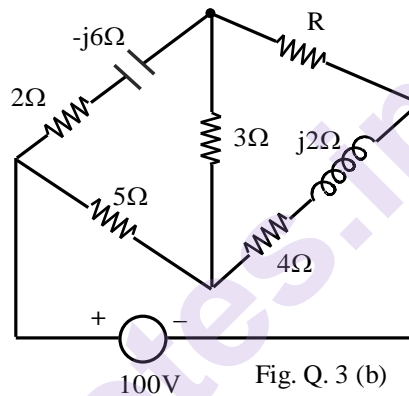


Fig. Q. 3 (b)

OR

4. a) Using Thevenin's theorem determine current through 6Ω resistance in the network of fig. Q. 4. 6

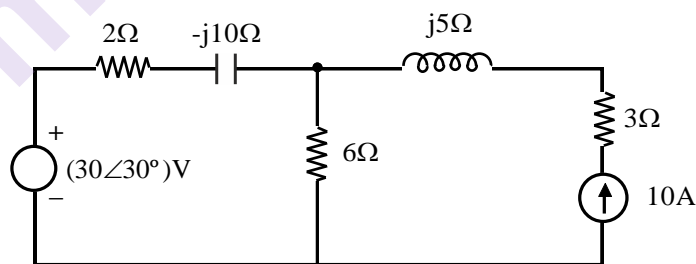


Fig. Q. 4 (a)

- b) In the network of fig. Q.4, determine current through 6Ω resistance using Norton's theorem. 6
- c) State and prove Millman's theorem. 4
5. a) With the help of example explain. 8
- i) Tree
 - ii) Basic cut-set
 - iii) Tie-set.

b) For the network shown in fig. Q.5(b)

8

i) Draw oriented graph & select a tree

ii) Write incidence matrix

iii) Write basic cut-set matrix

iv) Write tie set matrix.

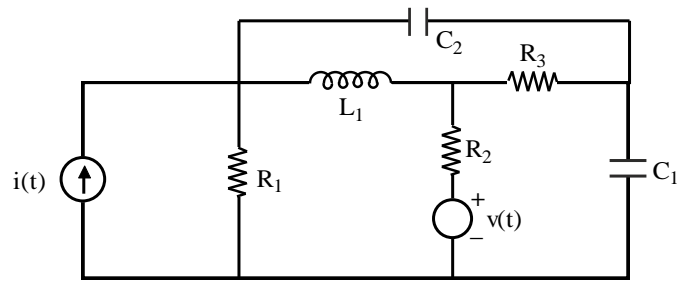


Fig. Q. 5(b)

OR

6. a) Find the trigonometric Fourier series for the triangular even waveform shown in fig. Q. 6.

8

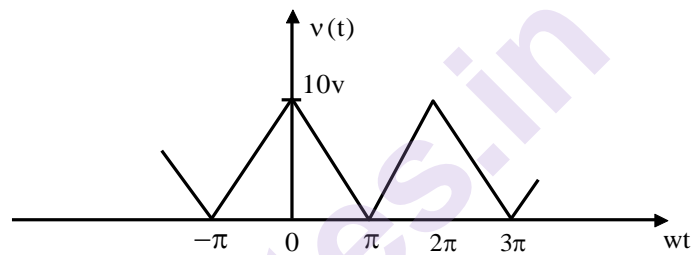


Fig. Q. 6

b) Determine the exponential form of Fourier series expansion for the periodic waveform shown in fig. Q. 6.

8

7. a) For the network function given below, draw the pole-zero diagram and using the pole-zero diagram obtain the time domain response

8

$$I(s) = \frac{4(s+2)s}{(s+1)(s+3)}$$

b) State the prove final value theorem prove final value theorem for the following functions-

8

i) $6 \cdot (1 - e^{-t})$

ii) $2 + e^{-3t} \cdot \cos 2t$

OR

8. a) Find the Laplace Transform of a periodic waveform shown in fig. Q. 8 (a).

8

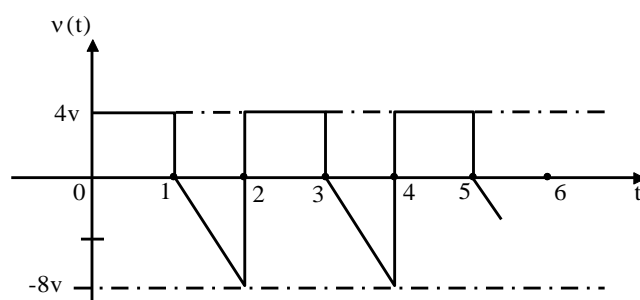


Fig. Q. 8 (a)

- b) In the network shown in fig. Q8(b), switch S is closed and steady state is reached. Now at $t = 0$, switch S is opened obtain the expression for current through the inductor at $t > 0$. Use Laplace transform method. 8


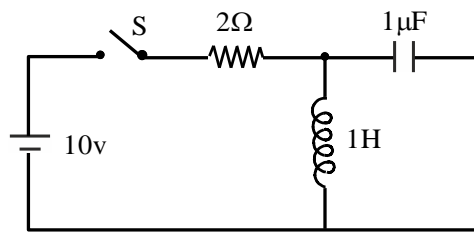


Fig. Q. 8 (b)

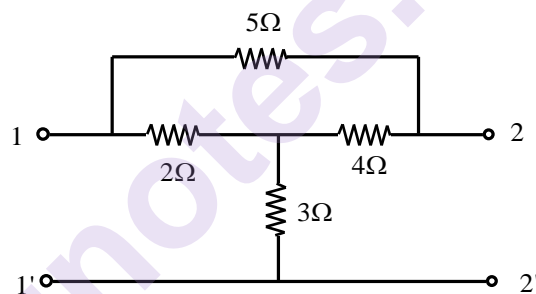9. a) A network is characterized by the following equations. 8
 $I_1 = 0.5 V_1 - 0.25 V_2$
 $I_2 = -0.25 V_1 + 0.625 V_2$
 Determine Z-parameters and ABCD parameters of the network.
- b) Find short circuit admittance parameters of the Network given in fig. Q.9 (b). Comment on reciprocity and symmetry of the network. 8



OR

10. a) A 400V, three phase star connected system has phase sequence RBY. The load connected in star has impedances 8
 $Z_R = (30 + j40)\Omega$, $Z_Y = (6 - j10)\Omega$, $Z_B = 100\Omega$.
 Find line currents. Also calculate the total power consumed by the load.
- b) Find hybrid parameters of the network given in fig. 10(b) and hence find Z parameters. Comment on reciprocity and symmetry. 8

