

**B.E. Electrical (Electronics & Power) Engineering / Electronics Engineering / Electronics & Telecommunication / Comm. Engineering (CBCS Pattern) Third Semester CBCS (New)**  
**3BEEE04 / 3BEEN02 / 3BEET03 : Electronics Devices & Circuits**

P. Pages : 3

Time : Three Hours




**GUG/W/18/11489**

Max. Marks : 80


- Notes :
1. All questions carry marks as indicated.
  2. Due credit will be given to neatness and adequate dimensions.
  3. Assume suitable data wherever necessary.

 1. a) Derive the V – I relationship of P – N Junction diode. 8  
 b) The saturation currents of two Zener diodes in the circuit are  $1\mu\text{A}$  and  $2\mu\text{A}$  respectively. 8  
 The break down voltages of the diodes are same and equal to  $100\text{V}$ .  
 Calculate the current and voltage of each diode if  $V_i = 90\text{V}$  &  $V_i = 110\text{V}$ .



**OR**

 2. a) Explain how depletion layer is formed across P – N Junction. Define barrier potential? 4  
 b) Explain Zener diode as voltage regulator. 4  
 c) A,  $120\text{V}$ ,  $60\text{Hz}$  voltage is applied to primary of  $5:1$  step-down transformer whose secondary is centre-tapped allowing a load of  $1\text{K}\Omega$  be connected to a full-wave rectifier utilizing two diodes. Neglecting voltage drop across two diodes. Determine : 8  
 i) The d.c. voltage across the load.  
 ii) d.c. current through the load.  
 iii) % efficiency.  
 iv) PIV of each diode.
3. a) Explain Base – Width modulation in BJT. 4  
 b) For the ckt shown in fig. 8




Show that Q is working in Saturation region. Also find currents.

- c) What is mean by biasing? Why there is need of biasing? Explain. 4

**OR**

 
4. a) Derive the hybrid parameters for. C – E configuration and draw the hybrid model. 8  
b) For the ckt shown in fig. 8  
Find  $A_I$  &  $A_{V_S}$ .



5. a) Define thermal resistance & Derive the expression for condition of thermal stability in self bias ckt. 8  
b) A Si- transistor with  $\beta = 50$ ,  $V_{BE(akt)} = 0.7V$ ,  $V_{CC} = 22.5V$  &  $R_C = 5.6K\Omega$  is used in voltage divider bias ckt. It is desired to establish Q. pt. at  $V_{CE} = 12V$  &  $I_C = 1.5mA$ . For stability factor  $S \leq 3$ , find  $R_1$ ,  $R_2$ , &  $R_e$ . 8


**OR**

 6. a) Draw the hybrid  $\pi$ - model of BJT in C – E connection & derive the expression for current gain. 8  
b) A BJT has  $g_m = 25mS$ ,  $r_{b'e} = 4.9K$ ,  $h_{ie} = 5\Omega$ ,  $r_{bb'} = 100\Omega$ ,  $c_{b'c} = 10pf$ ,  $c_{b'e} = 60pf$  and  $h_{fe} = 224$  at 1KHz. Calculate  $\alpha$  and  $\beta$  cut-off frequencies and  $f_T$ . 8
7. a) Differentiate between MOSFET and JFET. 4  
b) For JFET, if  $I_{DSS} = 20mA$ ,  $V_{GS(off)} = -5V$  and  $g_{mo} = 4mS$ . 4  
Determine transconductance for  $V_{gs} = -4V$  and  $I_D$  at that point.  
c) The amplifier shown has  $V_P = -2V$ ,  $I_{DSS} = 1.65mA$ . It is desired to bias the ckt at  $I_D = 0.8mA$  using  $V_{DD} = 24V$ . Assume  $r_d \gg R_d$ , find  $V_{gs}$ ,  $g_m$ ,  $R_s$  &  $R_d$  such that the voltage gain is at least 60 dB with  $R_s$  by passed with very large capacitance. 8



**OR**

 8. a) Explain the effect of temperature in MOSFEET with neat waveform. 8
- b) For the ckt shown below given that  $I_{D(ON)} = 6\text{mA}$ ,  $V_{GS(ON)} = 8\text{V}$ ,  $V_{gs(th)} = 3\text{V}$ . 8  
Calculate the values of  $I_D$  and  $V_{GS}$  at Q – point.



9. a) Draw the ckt of class B-push-pull amplifier. Obtain the condition for maximum power dissipation and hence show that  $P_{C(max)} = 0.4 P_{O(max)}$ . 8
- b) A transistor supplies 1W to  $5\text{K}\Omega$  load. A zero signal d.c. collector current is 35 mA and d.c. collector current with signal is 40 mA. Determine % second harmonic distortion. 8
- OR**
10. a) With neat ckt diagram, explain transformer, coupled class A push-pull Amplifier, how removes the problem of core saturation and eliminate even harmonics completely. 8
- b) Class B push pull amplifier is supplied with  $V_{CC} = 60\text{V}$  and signal to collector voltage down to  $V_{min} = 15\text{V}$ . The dissipation in both transistor totals 45W. Find : 8
- Load presented by O/P transformer.
  - Conversion efficiency.
  - Ratings of each transistor.

\*\*\*\*\*

[munotes.in](http://munotes.in)