

Bachelor of Science (B.Sc. -I) (CBCS Pattern) First Semester
USELT01 - Electronics Paper-I (Network Analysis and Digital Fundamentals)

P. Pages : 2

Time : Three Hours



GUG/W/18/11548


Max. Marks : 50

- Notes :
1. All questions are compulsory and carry equal marks.
 2. Draw neat and labelled diagram wherever necessary.
 3. Use of log table/calculator is allowed.

1. a) Explain the ideal voltage source and current source. How does ideal voltage source differ from practical voltage source? **6+4**
State Kirchhoff's current & voltage law.


OR

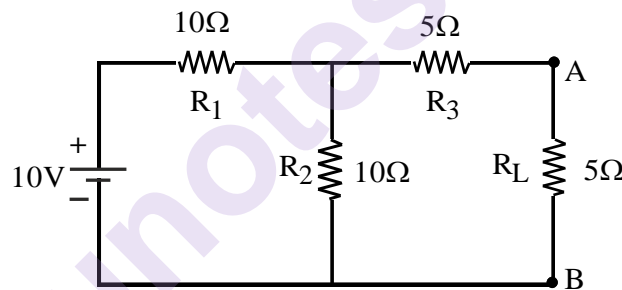- b) State and prove superposition theorem. Explain star and delta networks with suitable diagram. **6+4**
2. a) State and prove Thevenin's theorem. Using Thevenin's theorem, calculate the current flowing through resistor R_L in the following figure. **6+4**



OR

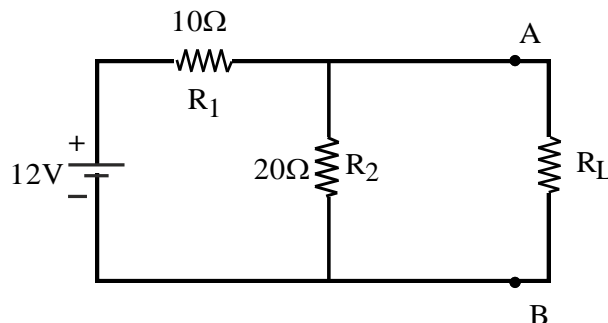- b) State and prove maximum power transfer theorem. **6+4**
Find the value of R_L to abstract maximum power from the circuit shown in following figure.



3. a) Explain the conversion method of decimal to binary number with suitable example. **6+4**
Perform the following conversion.
- i) $(120.20)_{10} = (\text{-----})_{16}$.
 - ii) $(101101101)_2 = (\text{-----})_8$.
 - iii) $(2A.14)_{16} = (\text{-----})_{10}$.
 - iv) $(101101101110100)_2 = (\text{-----})_{16}$.

OR

- b) Explain: **6+4**
i) 8421 code. ii) Excess-3 code
Perform the following arithmetic operation.
i) $(10111101)_2 + (11011010)_2 = (-----)_2$.
ii) $(10101110)_2 - (110101)_2 = (-----)_2$.

4. a) Why does NAND and NOR gate is called as universal gate? **2+8**
Construct the basic gates using NAND gate only and give its truth table.

OR

- b) State and prove DeMorgan's theorem for two variables and draw their logic diagram. **6+4**
Construct the XOR gate using basic gate. Give its truth table.

5. Attempt **any ten** of the following. **10x1**

- a) What is mesh?
- b) State principle of duality.
- c) What is difference between current source and voltage source.
- d) State Norton's theorem.
- e) What is two port network?
- f) Give any two notation of h-parameter.
- g) Define radix in number system.
- h) What is 1's complement?
- i) What is signed binary number?
- j) State the names of basic gates.
- k) Construct Ex-NOR gate using basic gate.
- l) Draw logic diagram of 4-bit Controlled inverter using XOR gate.
