Bachelor of Science (F.Y.B.Sc.) (PART-I) (CBCS Pattern) Second Semester CBCS USELT03 - Electronics Paper-I (Unipolar Devices and Linear Integrated Circuits)

P. Pages : 2 Time : Three Hour		2 ree Hours $* 3 6 5 3 *$	GUG/W/18/11578 Max. Marks : 50	
	Note	 All questions are compulsory and carry equal marks. Draw neat diagram wherever necessary. Use of log table/calculator is allowed. 		
1.	a)	Either. Distinguish between BJT and FET. Explain the construction and workin JFET.	g of N-Channel	3+7
		OR		
	b)	Explain the construction and working of UJT. Draw the V-I characterist explain.	cs of UJT and	6+4
2.		Either.		
	a)	Draw the circuit diagram of two stage RC coupled amplifier and explain Draw the frequency response curve.	its working.	7+3
		OR		
	b)	Define Barkhausen criterion for sustained oscillations. Draw and explain phase shift oscillator.	the working of	2+8
3.		Either.		
	a)	What are the advantages of operational amplifier over normal amplifier. Draw the circuit diagram of difference amplifier and explain its working		3+7
		OR		
	b)	Draw the block diagram of operational amplifier and explain the functio	n of each block.	10
4.		Either.		
	a)	Draw and explain the working of op-amp as an inverting amplifier. Expl of virtual ground.	ain the concept	7+3
		OR		
	b)	With suitable diagram explain the working of op-amp as an integrator.		3+7

- 5.
- Attempt **any ten** of the following.
- a) What is FET?
- b) What is pinch off voltage?
- c) State the advantages of MOSFET.
- d) Define Bandwidth of amplifier.
- e) What is oscillator?
- f) State formula of frequency for Colpitt's oscillator.
- g) State any two characteristics of Ideal op-amp.
- h) Define close loop gain in op-amp.
- i) State any two advantages of DC amplifier.
- j) What is unity gain amplifier?
- k) State the formula of output voltage of differentiator, using op-amp.
- 1) In Non-inverting op-amp $R_i = 10k\Omega$. and $R_f = 12k\Omega$. calculate the gain.
