



- Notes :
1. All questions are compulsory and carry equal marks.
 2. Draw neat and labelled diagrams wherever necessary.
 3. Avoid vague answers.

1. Either

- a) Write a brief note on. **8**
 - i) Excess 3 code
 - ii) Parity code
 - iii) Gray code
- b) What is Decimal Number System? Convert decimal to binary equivalent number with Example. **8**

Convert the following.

 - i) $(85)_{10} = ()_2$
 - ii) $(26)_{10} + ()_2$

OR

- c) What is BCD code? Why BCD code is called weighted code, Explain with example. also state its advantages and disadvantages. **8**
- d) Write in detail about real number representation. **8**

2. Either

- a) Give the truth table for. **8**
 - i) NAND
 - ii) NOR
 - iii) NOT
 - iv) AND
- b) Explain 2's complement in brief with suitable example. Also write steps and example for binary subtraction using 2's complement. **8**

OR

- c) Explain Binary Addition and subtraction in brief with suitable example. **8**
- d) Why NOR and NAND gates are called as universal gates? Explain in detail. **8**

3. Either

- a) What is Boolean algebra? Explain the laws and Identities of Boolean algebra. **8**
- b) What is K-Map? Explain K-map for 2,3,4 variables in brief. **8**

OR

- c) Write a brief note on. **8**
 - i) Multiplexer.
 - ii) Demultiplexer.

d) Explain Demorgan's Theorem in brief . 8

4. Either

a) Explain in detail the construction and working of RSFF. Give its truth table and timing diagram. 8

b) Write a brief note on. 8

i) Asynchronous counter.

ii) Synchronous counter.

OR

c) Explain the Johnson counter with its timing diagram in brief. 8

d) Explain DFF, TFF and JKFF in detail with its timing diagram. 8

5. Attempt all the questions.

a) Explain positive and Negative Number representation in detail with suitable example. 4

b) Write a brief note on 9's complement. 4

c) Explain POS and SOP logic expressions using K-map. 4

d) What is Ring counter? Explain with its timing diagram. 4
