

Bachelor of Science (F.Y.B.Sc.) First Semester
E-02 - Electronics Paper-II (Transducers and Network Theorems)

P. Pages : 2

Time : Three Hours



GUG/W/18/1207

Max. Marks : 50

- Notes :
1. All questions are compulsory and carry equal marks.
 2. Draw a neat diagrams wherever necessary.
 3. Use of log table/calculator is allowed.

1. Either

a) What is transducer?

1+6+3

Explain active and passive transducer with suitable example. Give the classification of transducer on the basis of quantities to be converted.

OR

b) What is LVDT?

6+4

Explain construction and working of LVDT with suitable diagram. Draw its characteristics and explain.

2. Either

a) What is solar cell?

5+5

Explain the construction and working of solar cell.
Explain construction and working of LDR.

OR

b) Explain the working of LASER diode with suitable diagram.
Explain the construction and working of LED.

5+5

3. Either

a) Explain ideal and practical voltage source. Draw its characteristics.
Define: Mesh, node and loops in networks.


7+3

OR

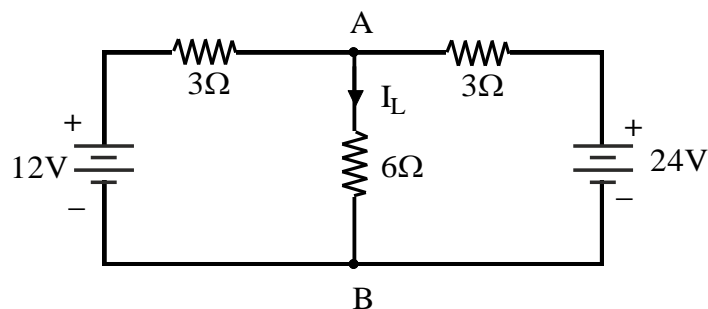
b) State and explain the superposition theorem.

4+6

Using superposition theorem, find the current through 6Ω resistor in the following circuit.




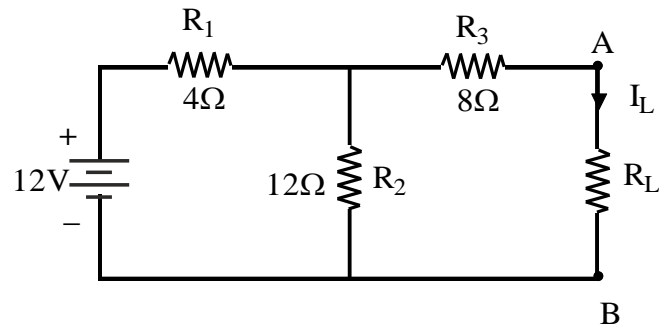4. Either
- a) State and prove Thevenin's theorem. Using Thevenin's theorem find the current through R_L in the following circuit. 6+4



OR

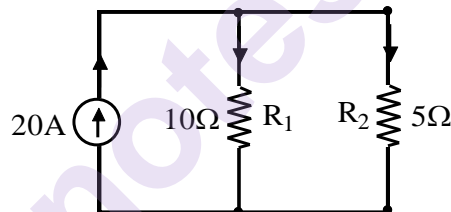- b) State and prove Millman's theorem. State and explain Maximum transfer theorem. 5+5
5. a) Explain the construction of loudspeaker. 2½
- b) Explain the operation of photovoltaic cell. 2½
- c) Find the current through R_1 and R_2 using current divider method in the following circuit. 2½



- d) State and explain Norton's theorem. 2½
