

## Bachelor of Science (S.Y.B.Sc.) (Part-II) Fourth Semester

## B.Sc. 24131 - Electronics Paper-I

## (Power Amplifiers, Oscillators and Power Supplies)

**GUG/W/18/1288**

\* 1 0 0 1 \*

Max. Marks : 50

- Notes :
1. All questions are compulsory and carry equal marks.
  2. Draw neat and well labelled diagram wherever necessary.
  3. Use of log table/calculator is allowed.

- |           |    |  |                         |
|-----------|----|--|-------------------------|
| <b>1.</b> | a) | Explain:<br>i) Voltage Amplifier<br>ii) Power Amplifier  | <b>4+6</b>              |
|           |    | Draw the circuit diagram of transformer couple class A amplifier and explain its working.<br><b>OR</b>   |                         |
|           | b) | Explain the working of class B push pull amplifier with suitable circuit diagram.<br>What is cross over distortion? How does it can be removed?  | <b>5+2</b><br><b>+3</b> |
| <b>2.</b> | a) | Explain the construction and working of phase shift oscillator.<br>State its advantages.<br>If value $R_1 = R_2 = R_3 = 10\text{k}\Omega$ and $C_1 = C_2 = C_3 = 1\mu\text{F}$ , determine the frequency of phase shift oscillator.  | <b>6+2</b><br><b>+2</b> |
|           |    | <b>OR</b>  |                         |
|           | b) | Draw the circuit diagram of transistor Colpitts oscillator circuit and explain its working.<br>In Colpitts oscillator circuit, $C_1 = 1\mu\text{F}$ , $C_2 = 2\mu\text{F}$ and $L = 10\text{mH}$ . Find the frequency of oscillator. | <b>7+3</b>              |
| <b>3.</b> | a) | Draw the block diagram of regulated power supply and explain each blocks.<br>State the advantages of Regulated Power Supply.<br><b>OR</b>  | <b>7+3</b>              |
|           | b) | Define the following terms:<br>i) Load Regulation<br>ii) Line Regulation<br>Explain the working of Zener diode as a voltage regulator.<br>State its disadvantages.   | <b>2+6</b><br><b>+2</b> |
| <b>4.</b> | a) | Draw the functional block diagram of LM317 and explain each blocks.<br>Write its salient features.<br><b>OR</b>  | <b>7+3</b>              |
|           | b) | Draw the circuit diagram of dual power supply using IC7805 and 7905 and explain.<br>Differentiate between single power supply and dual power supply.   | <b>7+3</b>              |
| <b>5.</b> | a) | What is power transistor? Explain its need.  | <b>2½</b>               |
|           | b) | Explain Barkhausen criterion for oscillation.  | <b>2½</b>               |
|           | c) | What are the disadvantages of unregulated power supply? Draw the circuit diagram of unregulated dc power supply  | <b>2½</b>               |
|           | d) | State the advantage of three terminal IC voltage regulator.  | <b>2½</b>               |

\*\*\*\*\*