

Bachelor of Science (S.Y.B.Sc.) (Part-II) Fourth Semester
B.Sc. 24132 - Electronics Paper-II (Digital Electronics-II)

P. Pages : 1

Time : Three Hours



GUG/W/18/1289

Max. Marks : 50

- Notes :
1. All questions are compulsory. and carry equal marks.
 2. Draw neat diagrams wherever necessary.
 3. Use of log table / Calculator is allowed.

1. Either
- a) Explain the concept of shift register. 3+6
Draw the circuit diagram of 5150 shift register and explain its working. +1
Give its application.
- OR**
- b) Draw the block diagram of Semiconductor memory. Explain its read and write operation. 5+5
Obtain 8 kbyte memory using 2 kbyte Draw a suitable diagram.
2. Either
- a) Explain the construction and working of 8x4 diode matrix ROM with Truth table. 6+4
Differentiate between Bipolar and MOS RAM.
- OR**
- b) Explain the working of dynamic RAM cell with suitable diagram. 5+5
Explain the construction and working of Charge Couple Device (CCD).
3. Either
- a) Explain the need of A/D and D/A converter in digital system. 4+6
Define following parameters of D/A converter.
i) Range ii) Resolution.
iii) Linearity. iv) Speed.
- OR**
- b) State the limitation of weighted type D to A converter. 4+4
Explain the construction and working of R-2R ladder D to A converter. +2
Derive the expression for its output voltage.
4. Either
- a) Explain the construction and working of counter type analog to digital converter, with 7+3
timing diagram.
State its limitations.
- OR**
- b) Draw the block diagram of digital frequency meter. Explain the working of each 4+6
functional blocks.
5. a) Differentiate between volatile and non volatile memory Give its example. 2½
x4
- b) State the advantages and disadvantages of dynamic RAM.
- c) Explain the concept of data acquisition system.
- d) Draw the circuit diagram of digital clock and explain its principle.
