

B.E. Computer Science & Engineering Fourth Semester
CS402 - Digital Circuits and Fundamentals of Microprocessor

P. Pages : 2

Time : Three Hours



GUG/W/18/1540

Max. Marks : 80

- Notes :
1. All questions carry marks as indicated.
 2. Assume suitable data wherever necessary.
 3. Illustrate your answers wherever necessary with the help of neat sketches.

1. a) Do as directed -
- i) $(ABCD.12)_H = (?)_8 = (?)_{BCD}$ 2
 - ii) $(4.236)_D = (?)_B = (?)_H = (?)_{\text{excess}-3}$ 3
 - iii) $(100011101.00010)_2 = (?)_D = (?)_H = (?)_8$ 3
- b) Implement the EX-OR gate using :
- i) NOR Gate only
 - ii) NAND Gate only
- OR**
2. a) Simplify the following functions using k-map. 8
- i) $f(A, B, C, D) = \sum m(0, 1, 4, 5, 7, 8, 9, 11) + d(2, 12, 13)$
 - ii) $f(A, B, C, D) = \bar{A}\bar{B}\bar{C}D + A\bar{B}\bar{C} + \bar{A}B\bar{C} + \bar{A}\bar{B} + AC$
- b) State and prove Demorgan's theorem. 8
3. a) Design a combinational circuit such that the 4-bit binary will appear at its input terminal and will generate an output which will be high if the input number is prime number. 8
- b) What is full adder. Design and explain the working with the help of truth table and logic equation. 8
- OR**
4. a) Implement the following function using suitable multiplexer. 8
- $f(A, B, C, D) = \sum m(0, 1, 3, 6, 8, 9, 11, 13)$
consider B as a input line and A, C, D as a selection lines to the multiplexer.
- b) What is parity generator ? Design a 3-bit odd parity generator and checker. 8
5. a) Convert SR flip-flop to JK flip-flop. 8
- b) Draw the logic diagram of master-slave JK flip-flop and explain the working. How master-slave JK flip-flop overcome from the condition of race around ? Explain. 8

OR

