B.E. Electronics Engineering Fourth Semester EN 402 - Digital Circuits and Fundamentals of Microprocessors

	ages : le : Thi	2 ree Hours * 1 2 2 4 *	GUG/W/18/1555 Max. Marks : 80		
	Note	2. Due credit will be given to neatness and adequate dimensions. 3. Assume suitable data wherever necessary. 4. Illustrate your answer wherever necessary with the help of neat s	sketches.		
1.	a)	Expand $A + B\overline{C} + AB\overline{D} + ABCD$ to minterms and simplify using k-map.	8		
	b)	Minimize using k-map and reduce using NAND gates only. $F(A, B, C, D) = \sum m (1, 2, 3, 8, 9, 11, 13, 15) + d(4, 5, 6, 14)$	8		
		OR			
2.	a)	What do you mean by cascading of parallel adder? Why it is required?	8		
	b)	Design 4 bit binary to excess-3 code converter.	8		
3.	a)	Design 2-bit magnitude comparator.			
	b)	Implement full adder circuit using two 4:1 MUX.			
		OR			
4.	a)	Draw the circuit for implementing 5:32 decoder using 3:8 and 2:4 decode	er combinations. 8		
	b)	Design a priority encoder with D ₂ having highest priority followed by D ₀	, D ₃ and D ₁ . 8		
5	a)	Explain with neat diagram the operation of 4-bit left shift register. Also g table and timing diagram.	ive the truth 8		
	b)	Draw the logic diagram of a S-R Latch using NOR gates and explain its of	operation. 8		
		OR			
6.	a)	Convert J-K flip flop to - i) D flip flop ii) T flip flop	8		
	b)	Design a type T counter goes through states 0, 3, 5, 6, 0. Is the counter se	lf starting. 8		
7.	a)	Explain the addressing modes of microprocessor 8085 along with example	e. 8		

	D)	addressing modes: i) PCHL	ii)	IN 73H	δ	
		iii) CALL 9000H	iv)	XCHG		
			O	R		
8.	a)					
	b)					
9.	a)	Draw and explain schematic structure of µp 8085 interrupt.			8	
b) Explain the format of SIM and RIM instruction.				on.	8	
OR						
10. a)		Draw and explain complete block diagram of 8255 PPI.			8	
	b)	Write an assembly language program to blink LED's on PCs pin. Initialise 8255 PPI with port A address 95H.			8	
