

**EN/ET/EC 501 - Linear Electronic Circuits / Linear Integrated Circuits**

P. Pages : 2

Time : Three Hours



**GUG/W/18/1621**

Max. Marks : 80

- Notes : 1. Questions carry marks as indicated.  
2. Assume suitable data wherever necessary.

1. a) Draw and explain the block diagram of operational amplifier. **8**  
b) Explain Dominant - pole frequency compensation technique for op-amp. **8**

**OR**

2. a) Draw and explain current mirror circuit used as constant current source. **8**  
b) Derive the equation for differential gain ( $A_{DM}$ ) using hybrid  $\pi$  model for transistorized differential amplifier when differential input signal is applied. **8**
3. a) Explain following op-amp parameters. **8**  
i) Input offset voltage. ii) CMRR  
iii) Slew rate. iv) Input bias current.  
b) Design a differentiator to differentiate an input signal that varies in frequency from 10Hz to about 1KHz. If a sine wave of 1V peak at 1000Hz is applied to this differentiator, draw its input-output waveforms. **8**

**OR**

4. a) Derive the output equation for integrator circuit. **8**  
b) i) For non-inverting amplifier circuit if  $R_F = 12k$ ,  $R_1 = 1k$ ,  $\pm V = \pm 15V$ . Find the output voltage for  $V_{in} = 250mV$  and  $V_{in} = 3V$ . **4**  
ii) For inverting amplifier circuit if  $R_F = 5k$ ,  $R_1 = 1k$ ,  $\pm V = \pm 15V$ . Find the output voltage for  $V_{in} = 0.5V$  and  $V_{in} = 7V$ . **4**
5. a) Draw and explain working of precision full wave rectifier circuit. **8**  
b) Draw and explain inverting Schmitt Trigger with neat circuit diagram. Also draw input output waveforms and voltage transfer curve for it. **8**

**OR**


6. a) Draw and explain square wave generator using op-amp. 8
- b) Draw and explain working of any negative voltage limiter circuit. 8
7. a) Draw circuit diagram of R-2R ladder DAC and write its output equation. 8
- b) Design second order Butterworth low pass filter having upper cut-off frequency of 1kHz. 8

OR

8. a) Draw circuit diagram of binary weighted DAC and write its output equation. 8
- b) Explain wide Band reject filter using op-amp. 8
9. a) Draw and explain Astable multivibrator operation using IC 555 with help of neat circuit diagram and waveforms. 8
- b) Draw and explain frequency multiplier using PLL. 8

OR

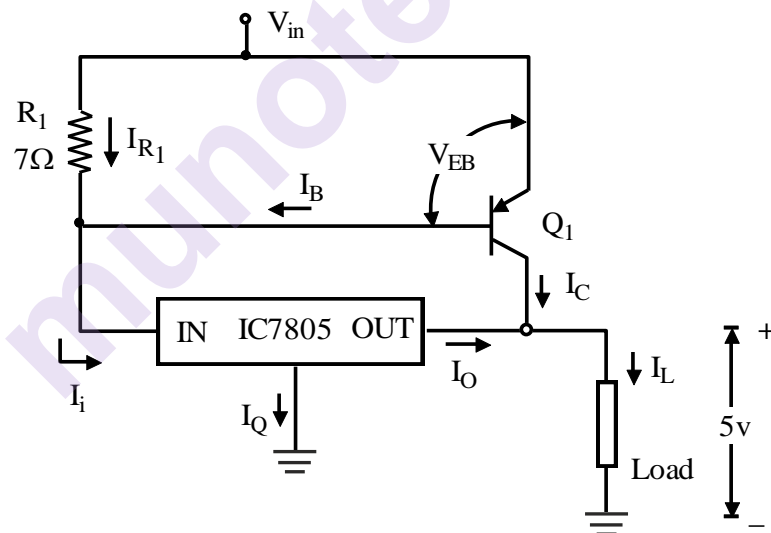10. a) If fig. shown, Let  $V_{EB(ON)} = 1V$  and  $\beta = 15$ . Calculate the output current coming from 1C7805 and  $I_C$  coming from transistor  $Q_1$  for loads  $100\Omega$ ,  $5\Omega$  and  $1\Omega$  8



- b) Calculate output frequency  $f_0$ , lock range  $\Delta f_L$  and capture range  $\Delta f_C$  of a IC565 PLL if  $R_T = 10k\Omega$ ,  $C_T = 0.01\mu F$  and  $C = 10\mu F$ . 8

\*\*\*\*\*