

M.Sc. (Physics) Third Semester Old
MSc231013 – Digital Electronics & Microprocessors Paper – XIII

P. Pages : 2

Time : Three Hours



GUG/W/18/2314

Max. Marks : 80

Notes : All questions are compulsory and carry equal marks.

1. Either :

- a) Explain TTL and CMOS circuits with reference to fan in / fan out, noise, speed, power dissipation with suitable examples. **10**
- b) Discuss half adder and full adder by using k – map. **6**

OR

- e) Explain ALU with emphasis on IC – 74181 in details. **8**
- f) State different methods of number representation. Draw the logic diagram of 8 bit binary adder using IC 7483 and explain its working. **8**

2. Either :

- a) Define multiplexer. Give the logic diagram and truth table for 4 : 1 multiplexer. **6**
- b) Implement the expression using a multiplexer **2**
 $f(A, B, C, D) = \sum m(0, 2, 3, 7, 9, 12, 14)$
- c) Define demultiplexer. Give the logic diagram and truth table for 1 : 8 demultiplexer. **6**
- d) Draw a pin layout of IC 74153 and give use of strobe pin. **2**

OR

- e) What is pulse amplitude modulation? Explain the channel bandwidth for pulse amplitude modulation. **8**
- f) Write notes on :
 - i) ASK **4**
 - ii) FSK **4**

3. Either :

- a) Discuss construction and working principle of CCD. Why is it called as an ideal detector. Explain three phase change transfer mode in it. **8**
- b) Discuss static and dynamic memory devices. **8**

OR

- e) Discuss architecture of IC 8086. 8
- f) What are A/D and D/A convertor? Explain R – 2R Ladder D/A converters. 8

4. Either :

- a) Discuss addressing modes including simple memory paging. 4
- b) Explain instruction execution fetch and execute cycle. 4
- c) Write a notes on immediate conditional jump shift. 4
- d) Explain change control and masking. 4

OR

- e) Discuss architecture of a microprocessor. What are the important components. 8
- f) Draw a Schematic diagram of a microprocessor. Discuss function of each components in brief. 8

5. Attempt all questions.

- a) Explain Don't care condition with suitable examples. 4
- b) Explain FDM and TDM in brief. 4
- c) Write notes on Magnetic bubble memories. 4
- d) Draw block diagram of IC 8155. 4
