

This question paper contains 4 printed pages]

Roll No.

| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|
| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|

S. No. of Question Paper : 106

Unique Paper Code : 32221303

I

Name of the Paper : Digital Systems and Applications

Name of the Course : B.Sc. (H) Physics CBCS

Semester : III

Duration : 3 Hours

Maximum Marks : 75

(Write your Roll No. on the top immediately on receipt of this question paper.)

Question No. 1 is compulsory. Attempt any four from the rest.

Attempt five questions in all.

(Non-programmable scientific calculators are allowed)

1. Answer any five of the following :

3×5

(a) Solve 11001 - 11100 using 2's complement method.

(b) Reduce the expression given below using Boolean Algebra

$$AB + \overline{AC} + \overline{ABC}(AB + C)$$

(c) What is the function of delay line in a C.R.O. ?

P.T.O.

- (d) Write Boolean expressions for the following circuit :



- (e) Define what is SSI, MSI, LSI in an IC.
- (f) Distinguish between synchronous and asynchronous counter.
- (g) Define ROM, PROM and EPROM.
- (h) List any *three* functions which a microprocessor performs.
2. (a) Explain with an appropriate logic circuit the working of a 4 bit adder subtractor. 7
- (b) Simplify the expression using K-Map and draw its logic circuit using NAND gates : 8

$$F = \sum m(0, 1, 4, 6, 8, 9, 11) + d(2, 7, 13)$$

3. (a) Draw the circuit for a monostable multivibrator using IC555 and explain its operation. Derive an expression for the time period of the output waveform. Give *one* application of monostable multivibrator. 8

- (b) Draw a labelled block diagram of CRO. What is the function of time-base circuit in CRO. How is the CRO used for frequency determination ? 7
4. (a) What are decoders ? Draw and explain the working of a 3 to 8 line decoder. 6
- (b) Draw the circuit of a 4 bit shift left register with parallel loading and explain its working. 5
- (c) What do you understand by parity ? Describe a method for generating odd parity. 4
5. (a) What is a flip flop ? Explain the working of RS flip flop. How the racing condition is avoided in a J K master slave flip flop ? 8
- (b) Design an asynchronous decade counter. Explain the working of a ring counter as a periodic switch. 7
6. (a) What is the function of the following : 4
- (i) Program counter
- (ii) Stack Pointer.
- (b) Describe different addressing modes available in 8085 microprocessor. Give *one* example of each addressing mode. 5

- (c) Describe the various flags used in 8085 microprocessor and show their bit position. What is the mnemonic of an instruction that uses AC flag. 6
7. (a) Write a program to add the two hex numbers : A5, 98. Store the sum in memory location 200AH and carry in 200BH. 4
- (b) Write the classification of instructions for 8085 μ P. Explain briefly different instructions of the branch group. 5
- (c) How is de-multiplexing of address and data buses done in 8085 μ P ? Explain with the help of timing diagram. 6