

10.12.18 (M)

[This question paper contains 4 printed pages.] ✓

Your Roll No.....

Sr. No. of Question Paper : 765

IC

Unique Paper Code : 32227505

Name of the Paper : Physics and Devices and
Communication

Name of the Course : B.Sc. (Hons.) Physics :
DSE-2

Semester : V

Duration : 3 Hours

Maximum Marks : 75

Instructions for Candidates

1. Write your Roll No. on the top immediately on receipt of this question paper.
2. Attempt **five** questions in all.
3. Question No. 1 is compulsory.
4. All question carry equal marks.

1. Attempt any **five** questions of the following :

(5×3=15)

(a) Draw the I-V characteristics of a UJT.

(b) Define positive and negative photo masking with suitable diagrams.

P.T.O.

- (c) Draw the small signal equivalent circuit of JFET.
- (d) Define line and load regulation of a power supply.
- (e) Distinguish between active and passive filters with examples.
- (f) What is the phase locked state in phase locked loop (PLL)?
- (g) Draw the block diagram for the implementation of RS232 on PC.
- (h) Calculate the power developed by AM wave in a load of 100 ohms when the peak voltage of the carrier is 100 V and modulation index is 0.6.
2. (a) Discuss with appropriate diagrams the phenomenon of accumulation, depletion and inversion of a real metal oxide semiconductor (MOS) device. (12)
- (b) Give the transfer characteristics of p-channel JFET. (3)
3. (a) Discuss the processes of diffusion and ion implantation of dopants in IC fabrication. (10)
- (b) Explain the phenomenon of wet etching with suitable example. (5)

4. (a) Using appropriate circuit diagram obtain the expression for the gain of an active low pass filter. (6)
- (b) Explain the working of voltage controlled oscillator. (6)
- (c) If $R = 1\text{ k}\Omega$ and $C = 0.1\text{ }\mu\text{F}$ for a low pass filter and $R = 10\text{ k}\Omega$ and $0.1\text{ }\mu\text{F}$ for a high pass filter. Calculate the centre frequency for a corresponding band pass filter. (3)
5. (a) Draw the circuit diagram of a diode detector and explain its working. (5)
- (b) What is analog modulation? Define modulation index and deduce the power relation between carrier and side bands in amplitude modulated wave? (10)
6. (a) Explain the working of a transistor based monostable multivibrator. (10)
- (b) Sketch the wave forms of amplitude shift keying and frequency shift keying. (5)
7. (a) What is handshaking? Distinguish between parallel and serial data communication. (5)

- (b) Briefly explain the reactive ion etching (RIE) technique. (5)
- (c) How the information is stored in a charge coupled device? (5)