

Question Paper Set No. : Set B

Roll No. ....

Name of Course : B.Sc. Hons. Physics-CBCS\_Core

Semester : IV- Semester

Name of the Paper: : Analog Systems and Application

Unique Paper Code : 32221403

Duration : 2 hours

Max. Marks : 75 marks

**Attempt FOUR questions in all All questions carry equal marks**

(Given :  $\epsilon_0 = 8.85 \times 10^{-12} \text{ F/m}$ ;  $k = 1.38 \times 10^{-23} \text{ J/K}$  ;  $q = 1.6 \times 10^{-19} \text{ C}$  )

Q1

This sample is doped with  $10^{14}$  donor *atoms/cm<sup>3</sup>* and  $5 \times 10^{13}$  acceptor *atoms/cm<sup>3</sup>*. The resistivity of pure Ge is  $65 \Omega\text{-cm}$  at the room temperature. Find the total current density if the applied electric field is  $2.2 \text{ V/cm}$ . (Given  $\mu_N = 3800 \text{ cm}^2 \text{V}^{-1} \text{s}^{-1}$  and  $\mu_P = 1800 \text{ cm}^2 \text{V}^{-1} \text{s}^{-1}$ )

In a *pn*-junction diode,  $J$  is the total current density when a forward bias voltage  $V$  is applied across it. Determine the relationship between  $J$  and  $V$ .


An abrupt *pn* junction at  $27^\circ \text{C}$  is doped with acceptor concentration of  $5 \times 10^{16} \text{ atoms/cm}^3$  and donor concentration of  $8 \times 10^{15} \text{ atoms/cm}^3$ . Determine the capacitance per unit area of the device if a reverse bias of  $0.2 \text{ V}$  is applied across the diode. (Given  $\epsilon_r = 11.7$  ;  $n_i = 1.5 \times 10^{10} \text{ per cm}^3$ ).

Q2

A full-wave bridge rectifier is to be designed to produce a peak output voltage of  $20 \text{ V}$  and  $180 \text{ mA}$  current to the load. An input line voltage of  $100 \text{ V (rms)}$ ,  $60 \text{ Hz}$  is available. Calculate the transformer turn ratio and the value of the capacitor to produce an output with a ripple of not more than 12 percent. Draw the complete circuit of the designed rectifier. (Assume the diode cut-in voltage as  $0.7 \text{ V}$ ).


List any two features of a pn-junction diode which exhibits a negative resistance region. Plot its I-V characteristics and explain with the help of energy band diagrams the conduction mechanism in the negative resistance region.

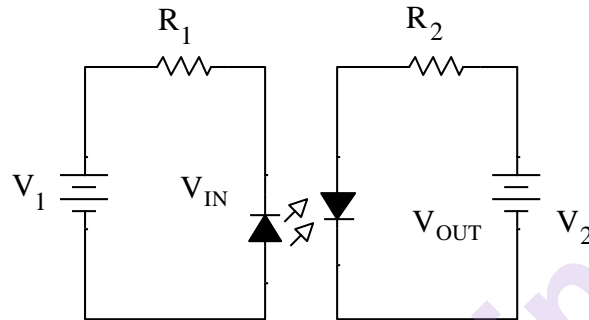Draw the I-V curve across both the types of diodes in the following figure.



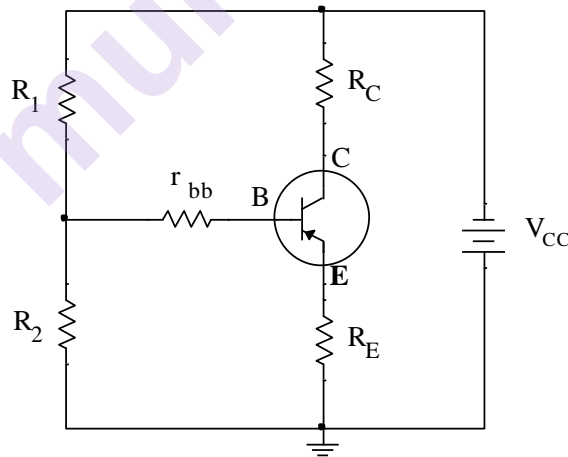**Q3**

Discuss how addition of emitter resistance stabilizes the voltage-divider bias circuit. The self-biased transistor as shown in figure below has following the specifications;  $V_{CC} = 4.5\text{ V}$ ,  $R_C = 1.5\text{ k}\Omega$ ,  $R_E = 0.27\text{ k}\Omega$ ,  $R_1 = 27\text{ k}\Omega$ ,  $R_2 = 2.7\text{ k}\Omega$  and  $\beta = 44$ . Find the value of the stability factor and also determine the Q-point when resistance  $r_{bb}$  is neglected, as well as when  $r_{bb} = 690\text{ }\Omega$  is taken into account.



**Q4**

For any transistor amplifier prove that


$$R_i = \frac{h_i}{1 - h_r A_v}$$

The following information is available for generalized feedback network. Open loop voltage amplification  $A_V = -100$ , input voltage of the system  $V_i = 1 \text{ mV}$ . Determine closed loop voltage amplification, output voltage, feedback voltage, input voltage to amplifier and type of feedback for  $\beta = 0.01$ . Also determine percentage variation in closed loop voltage amplification resulting from 100 percent increase in open loop voltage amplification.

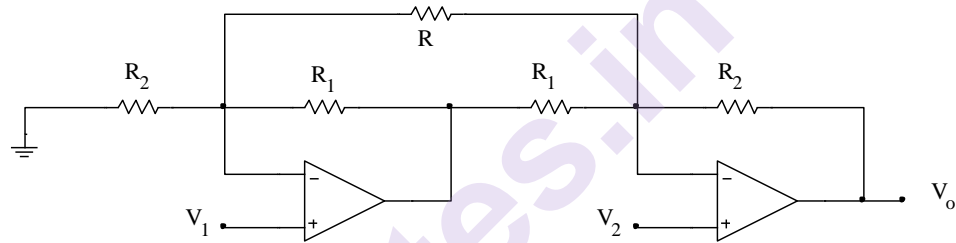Q5


For the circuit shown below show that

$$V_o = \left(1 + \frac{R_2}{R_1} + \frac{2R_2}{R}\right)(V_2 - V_1)$$




Deduce an expression for the frequency of oscillations for the circuit below if
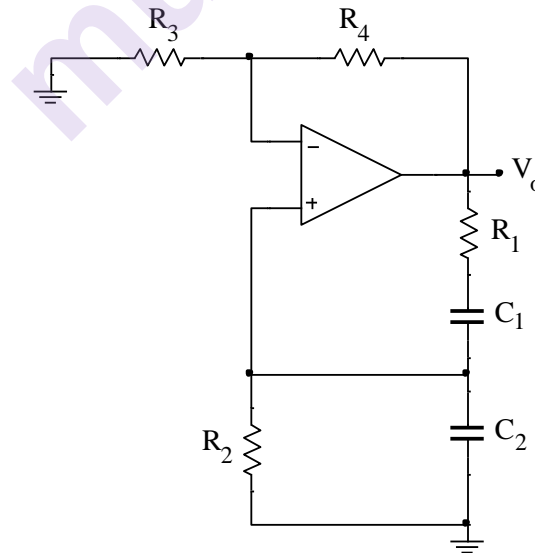
$$R_1 = R_2 = 1.5 \text{ k}\Omega ; R_3 = 1 \text{ k}\Omega ; R_4 = 2 \text{ k}\Omega ; C_1 = C_2 = 4.7 \text{ }\mu\text{F}$$



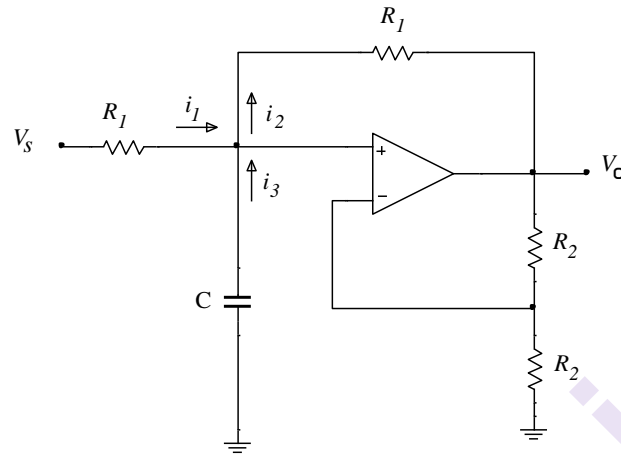Q6

For the circuit given below determine the relation between  $V_o$  and  $V_s$ . Also comment on the function of the circuit.



The output corresponding to a digital input 11001 and  $V_{ref} = 10V$  of an op-amp based 5-bit binary weighted DAC is fed to the inverting terminal and an  $ac$  signal  $10 \sin 100\pi t$  volts is fed to the non-inverting terminal of another op-amp as shown in the figure. Show the complete circuit of the DAC if  $R_F = 1k\Omega$  and  $R = 32k\Omega$ . Also determine the output  $V_o$  and draw its waveform.

