

1353

4

7. Write short notes on the followings : (5,5)

(a) Digital storage Oscilloscope

(b) Digital multimeter

(1500)

[This question paper contains 4 printed pages.]

30 NOV 2022

Your Roll No.....

Sr. No. of Question Paper : 1353

Unique Paper Code : 32223904

Name of the Paper : Basic Instrumentation Skills

Name of the Course : B.Sc Prog CBCS_SEC
(Prog / Hons)

Semester : V/III

Duration : 3 Hours

Maximum Marks : 50

Instructions for Candidates

1. Write your Roll No. on the top immediately on receipt of this question paper.
2. Attempt any **five** questions in all. **All** questions carry equal marks.
3. Use of non-programmable scientific calculator is permitted.

1. (a) Describe the static characteristics of an instrument.
Explain the difference between accuracy and precision of a measurement with an example.

P.T.O.

- (b) What is limiting error? A voltmeter reads 70 V on its 100 V range and an ammeter reads 80 mA on its 150 mA range are used to determine the power dissipated in a resistor. Both these instruments are guaranteed to be accurate within $\pm 1.5\%$ at full scale deflection. Determine the limiting error of the power. (5,5)
2. (a) Explain the principle of voltage measurement of an ac millivoltmeter with block diagram. A basic D'Arsonval movement with a full-scale deflection of $200 \mu\text{A}$ and internal resistance of 100Ω is used as a voltmeter. Determine the value of the multiplier resistance needed to measure a voltage of range 0-50 V.
- (b) Explain the operation of full wave rectifier type AC voltmeter with a suitable diagram. (5,5)
3. (a) Draw the block diagram of a Cathode Ray Oscilloscope (CRO) and explain the functions of each block.

- (b) Distinguish between dual beam and dual trace CRO. (5,5)
4. (a) Explain the operation of Schering bridge to determine the unknown Capacitance and also derive the relevant balancing equations.
- (b) A Wein bridge at balance has the following components given as: $R_1 = R_2 = 820 \Omega$, $C_1 = 0.2 \mu\text{F}$, $C_2 = 0.4 \mu\text{F}$, and $R_3 = 1.5 \text{ k} \Omega$. Determine the frequency of the bridge. (5,5)
5. (a) Describe the working of a Q-meter for measurement of high impedance value.
- (b) What is distortion factor meter. Explain its working. (5,5)
6. (a) Draw the block diagram of a pulse generator and explain its operation.
- (b) What is a universal counter? How can it be used to measure the frequency, time and period. (5,5)