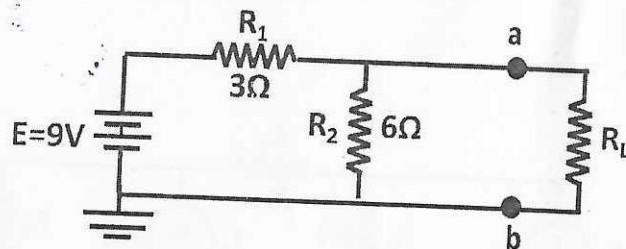


1244

8



(5)

(1000)

[This question paper contains 8 printed pages]

Your Roll No.

21 JUL 2023

Sr. No. of Question Paper : 1244

Unique Paper Code : 2222011203

Name of the Paper : Electrical Circuit Analysis
(DSC-6)

Name of the Course : B.Sc. (Hons.) Physics

Semester : II

Duration : 2 Hours

Maximum Marks : 60


Instructions for Candidates

1. Write your Roll No. on the top immediately on receipt of this question paper.
2. All questions carry **equal marks**.
3. **Question No. 1** is compulsory and attempt **any three** from the remaining four questions.
4. Use of non-programmable scientific calculator is allowed.

P.T.O.

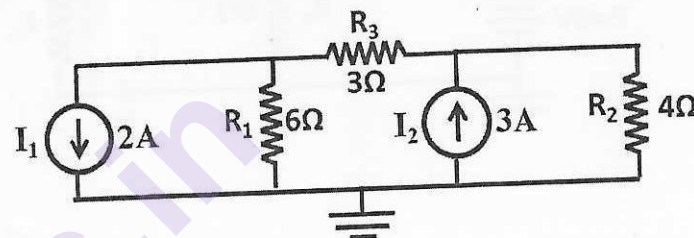
1. Attempt all questions. Each question carries equal marks. (3x5=15)

- Determine the form factor and peak factor for a half-rectified sinusoidal wave.
- What is the principle of duality in network analysis?
How can it be used to solve problems in network analysis?
- Calculate average and rms values of the current,
 $i(t) = 10 + 10 \sin \omega t$.
- A $0.1 \mu\text{F}$ capacitor is first charged and then discharged through a $10\text{M}\Omega$ resistor. Find the time in which the potential will fall off half of its maximum value.



- (5)
A series RL circuit with $R = 560 \Omega$ and $L = 350 \text{ mH}$ is driven by a sinusoidal current source, $i(t) = 30 \cos(\omega t + 25^\circ)$ ampere, where $\omega = 1000 \text{ rad/s}$. Find the voltage drop across R and L and the input voltage. (5)
- (c) Find the Norton equivalent circuit at ab of the given network.

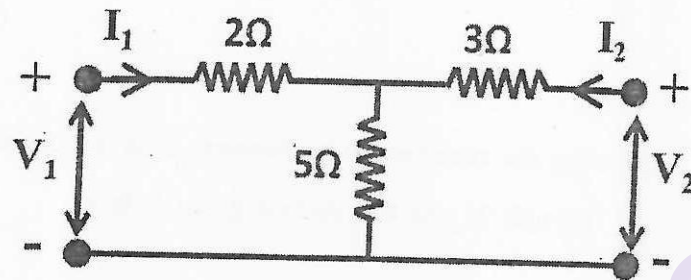- (b) Determine the transmission parameters (ABCD) of the given network.



(7)

5. (a) Determine the voltage across R_3 resistor using the nodal analysis method.

- (e) Discuss briefly how a voltage source can be converted into a current source and vice-versa.


2. (a) Derive an expression for resonance frequency of a series LCR circuit having an alternating voltage source. Calculate the resonant frequency and quality factor of the circuit for given values of $C = 550 \text{ nF}$, $R = 60 \Omega$ and $L = 260 \text{ mH}$ respectively. (8)

- (b) A series LCR circuit with $R = 6\Omega$, $X_L = 10\Omega$ and $X_C = 12\Omega$ is driven by a sinusoidal voltage source, $v(t) = 20 \cos(4000t)$ volts. Determine the equivalent impedance of the circuit. Also, draw its phasor diagram. (7)

1244

4

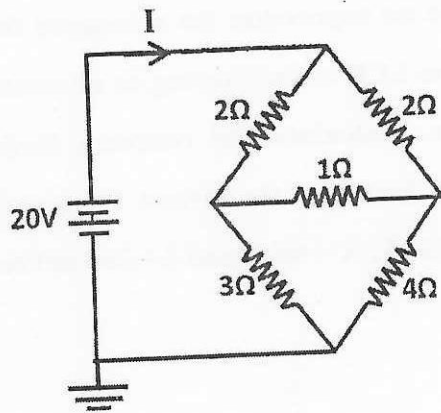3. (a) Determine the value of current I in the given diagram by using the Star-delta conversion method.




(8)

- (b) Find out source current I_s and current through the resistance 2Ω ($I_{2\Omega}$) in the circuit given below.


1244

5

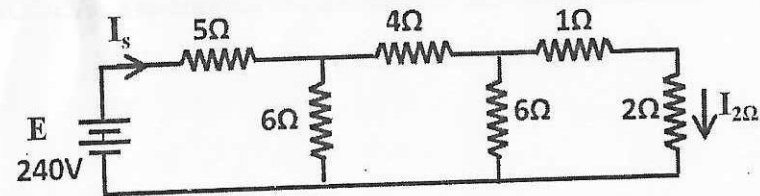

(7)

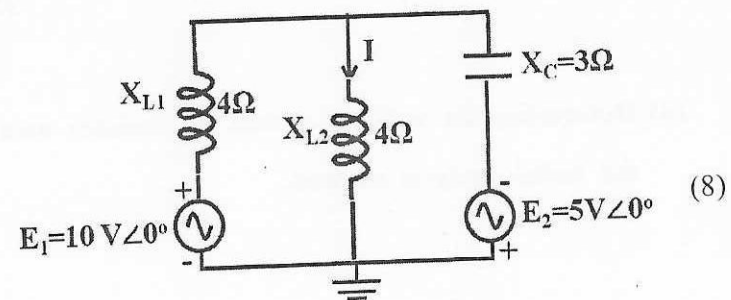4. (a) Using the superposition theorem, find the current I through X_{L2} in the circuit given below.



P.T.O.