

(3 Hours)

Total Marks: 80


N. B.1) Question No. 1 is compulsory.

- 2) Answer any 3 questions from the remaining 5 questions.
- 3) Assume suitable data wherever necessary.


Q1 Attempt any five of the following

20

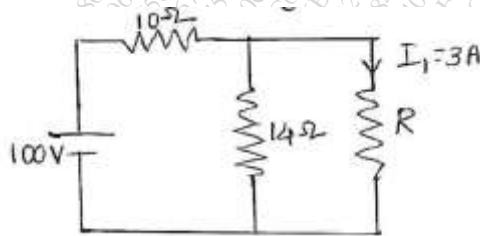
- (a) Explain the working principle of Single Phase Transformer.
- (b) Derive the formula to convert a Star circuit into equivalent Delta.
- (c) Explain the principle of operation of DC motor.
- (d) What is the necessary condition for resonance in series circuit? Derive the expression for resonance frequency.
- (e) Find the value of R in the following circuit.



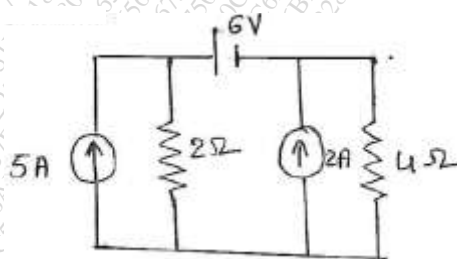- (f) Find the current through 4Ω resistor by source transformation in the following circuit;



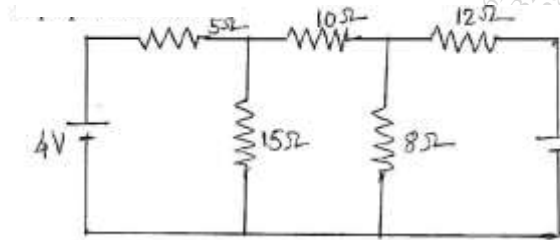- Q2 a) Determine the current through 8Ω resistor in the following Network by superposition theorem; 8



- (b) An Inductive coil having inductance of 0.04H and resistance 25Ω has been connected in series with another inductive coil of inductance 0.2H and resistance 15Ω . The whole circuit is powered with 230V , 50Hz mains. Calculate the power dissipation in each coil and total power factor. 8
- (c) What are the losses in transformer? Explain why the ratings of transformer in KVA not in KW 4
- Q3 (a) With necessary diagrams prove that three phase power can be measured by only two wattmeters. Also prove that reactive power can be measured from the wattmeter reading. 10
- (b) An alternating voltage is represented by $v(t) = 141.4 \sin(377t)$ V, Derive the RMS value of the voltage. 10

Find

- i) Instantaneous voltage value at $t = 3\text{ms}$
- ii) The time taken for voltage to reach 70.7 V for first time.

- Q4 (a) State and prove Maximum power transfer Theorem. 8

- (b) A 5KVA $1000/200\text{V}$, 50 Hz Single phase transformer gave the following test result 12


OC TEST(hv side):	1000V	0.24A	90W
SC TEST(hv side) :	50V	5A	110W

Calculate

- i. Equivalent circuit for transformer with circuit constant
 - ii. Regulation at full load at 0.8 lagging
 - iii. kVA load for maximum efficiency.
- Q5 (a) Three similar coils each having a resistance of 10Ω and inductance 0.04H are connected in star across 3-phase 50Hz , 200V supply. Calculate the line current, total power absorbed, reactive coil amperes and total volt amperes. 8

- (b) In the following circuit find R for maximum power delivered to it. Also find maximum power delivered P_{max} .

8

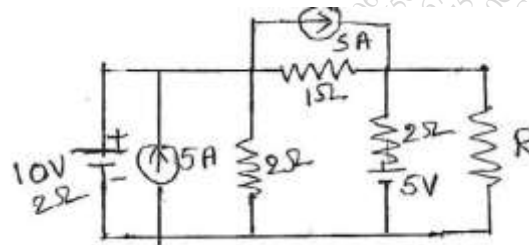


- (c) Two impedances $12+j16\Omega$ and $10-j20\Omega$ are connected in parallel across 230V, 50Hz Single phase ac supply. Find kW, kVA and kVAR and Power factor.

4

- Q6 (a) Draw and Explain the phasor diagram for the practical transformer connected to lagging power factor.
 (b) Find i) average value ii) rms value.

6

10

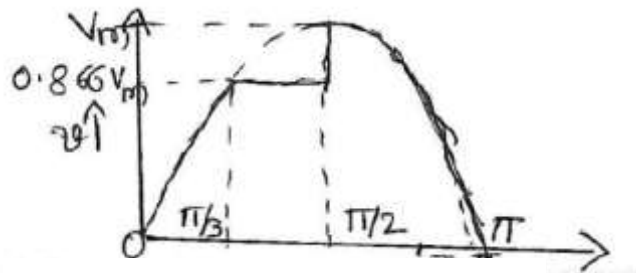

- (c) State and Explain Thevenin's theorem and Norton's theorem

4