(3 hours) [Total Marks: 80]

Note:

- 1. Question-1 is compulsory.
- 2. Answer any three questions from remaining five.
- 3. Assume suitable data if necessary.
- 4. Numbers in the right indicate marks.
- 1. Answer the following questions. (Each question carry 5 marks)


20

- (a) Distinguish between linear valve and equal percentage valve.
- (b) Draw circuit diagram of a basic RC band-pass filter. Sketch its frequency response clearly showing the expressions for cut-off frequencies.
- (c) Describe any two discontinuous controller modes.
- (d) What are two PLC operation modes? Describe both modes in brief.
- **2.** (a) Draw basic pneumatic system and describe its components.

10

10

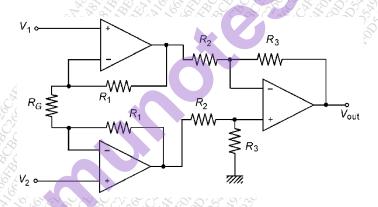- (b) Illustrate the working of V-to-I and I-to-V converters with neat circuit diagrams.
- 3. (a) Consider the instrumentation amplifier shown in figure below. Derive the expression for V_{out} and compute the resistors for the gain of 101.



- (b) What are the criteria for selecting controller mode for a given process? Describe the ratio controller with clearly specifying the types of processes for which it is used.
- 4. (a) An integral controller is used for speed control with a setpoint of 12 rpm within a range of 10 to 15 rpm. The controller output is 22% initially. The integral gain $K_I = -0.15\%$ controller output per second per percentage error. If the speed jumps to 13.5 rpm, calculate the controller output after 2s for a constant e_p .
 - (b) Draw the basic structure of PLC and describe its components in detail. 10

[TURN OVER]

Paper / Subject Code: 42551 / Instrumentation System Design

- **5.** (a) Develop the physical ladder diagram for a motor with the following: NO 10 start button, NC stop button, thermal overload limit switch opens on high temperature, green light turns on when running, red light turns on for thermal overload.
 - (b) What is a Data Acquisition System (DAS)? Describe, with clear diagram, 10 working of a typical DAS.
- 6. Answer any two of the following questions.
 - 20
 - (a) Write a short note on SCADA.
 - (b) What is the scope of standard NEMA 250? Describe its features in brief.
 - (c) List any five SAMA symbols. Draw clear symbol with brief description.

